



JOINT INSTITUTE  
交大密西根学院

# ECE2150J Introduction to Circuits

## Chapter 5. Operational Amplifiers


Yuljae Cho, PhD  
Associate Professor  
UM-SJTU Joint Institute, SJTU


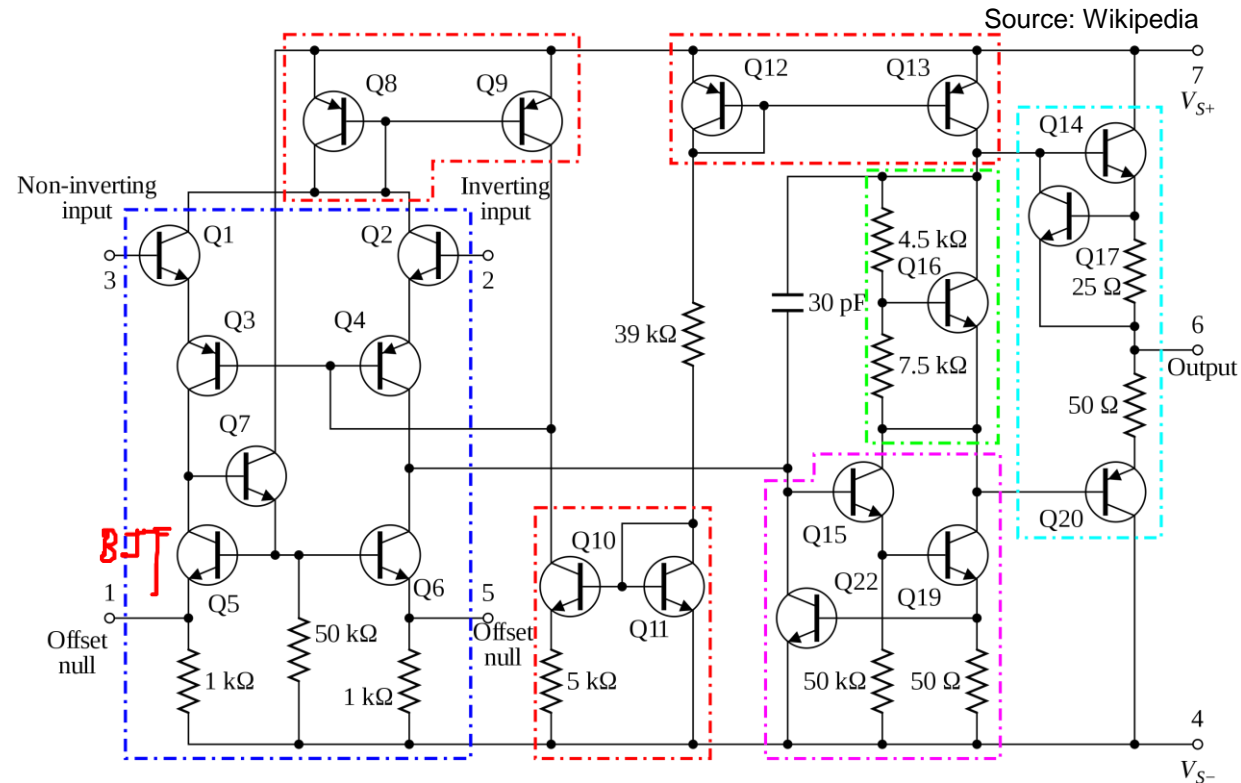
## 5.1 Introduction


The **operational amplifier**, or **op amp**, is an electronic device that behaves like a **voltage-controlled voltage source**. An op amp circuit can perform mathematical operations of *addition*, *subtraction*, *multiplication*, *division*, *differentiation*, and *integration*.

The op amp is an electronic device consisting of a **complex arrangement** of resistors, transistors, capacitors, and diodes




A component-level diagram of the common 741 op amp

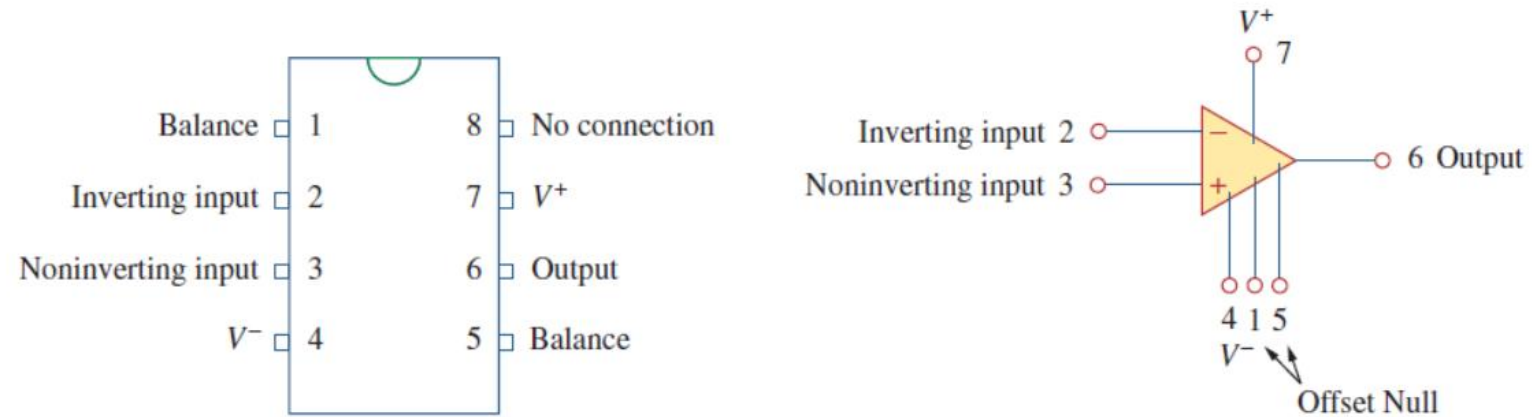What we would see in this textbook is this.



So don't be afraid of op amp


## 5.2 Operational Amplifiers

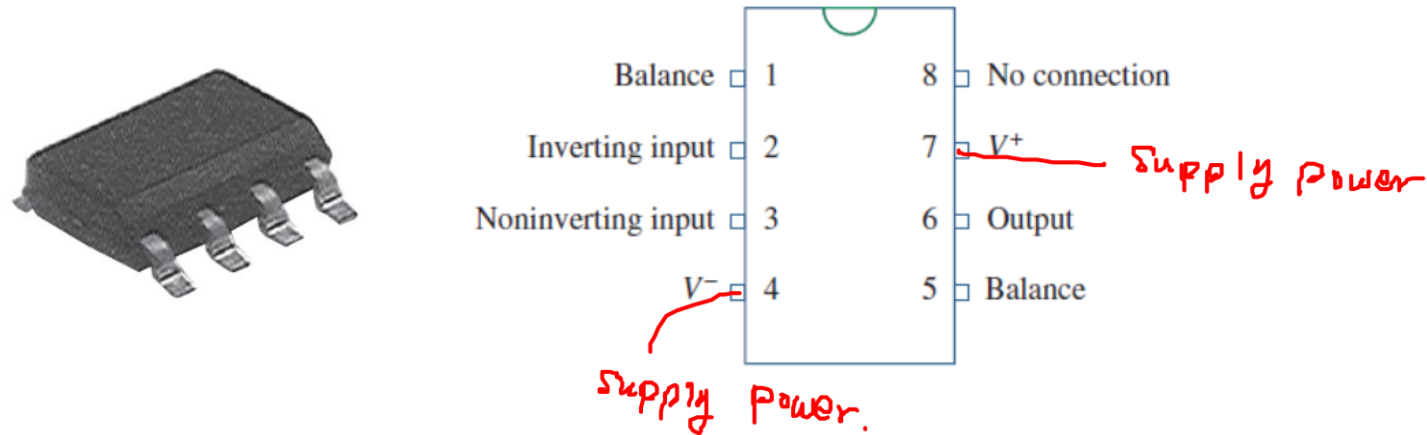


We treat the op amp as a circuit building block and **simply study what takes place at its terminals**. A full discussion of what is inside the op amp is in VE311.
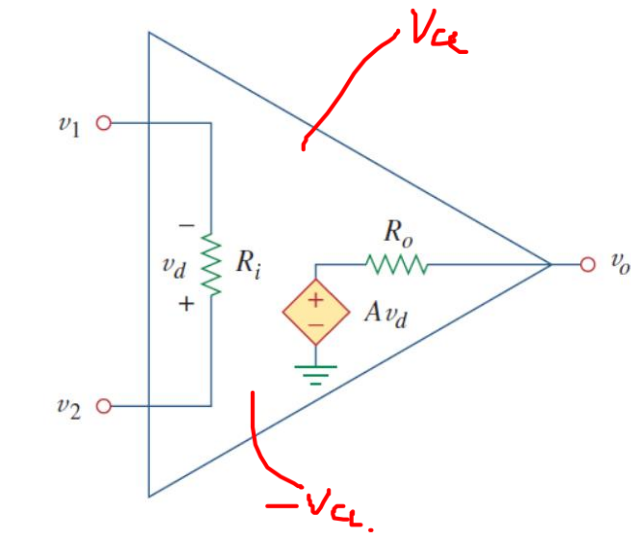
# What is Op Amp?

Op amp basically amplifies input voltage by the amount of a gain.



$$v_o = A v_d = A(v_2 - v_1)$$

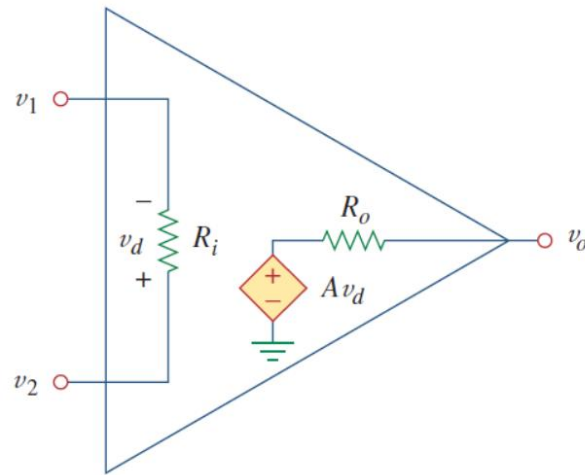

$$v_o = Av_d = A(v_2 - v_1)$$

$R_i$  is  $R_{Th}$  seen at the input.

$R_o$  is  $R_{Th}$  seen at the output.

The output  $v_o = Av_d = A(v_2 - v_1)$  where  $v_d$  is called the differential input voltage and  $A$  is called the open-loop voltage gain. It is the gain of the op amp without any external feedback from output to input.


**TABLE 5.1 Typical ranges for op amp parameters**

<i>Parameter</i>	<i>Typical range</i>	<i>Ideal values</i>
Open-loop gain, $A$	$10^5$ to $10^8$	$\infty$
Input resistance, $R_i$	$10^5$ to $10^{13} \Omega$	$\infty$
Output resistance, $R_o$	10 to 100 $\Omega$	0
Supply voltage, $V_{CC}$	5 to 24 V	NA



# Practical Limitation of Op Amp


The magnitude of its output voltage cannot exceed  $|V_{CC}|$ . In other words, the output voltage is dependent on and is limited by the power supply voltage.

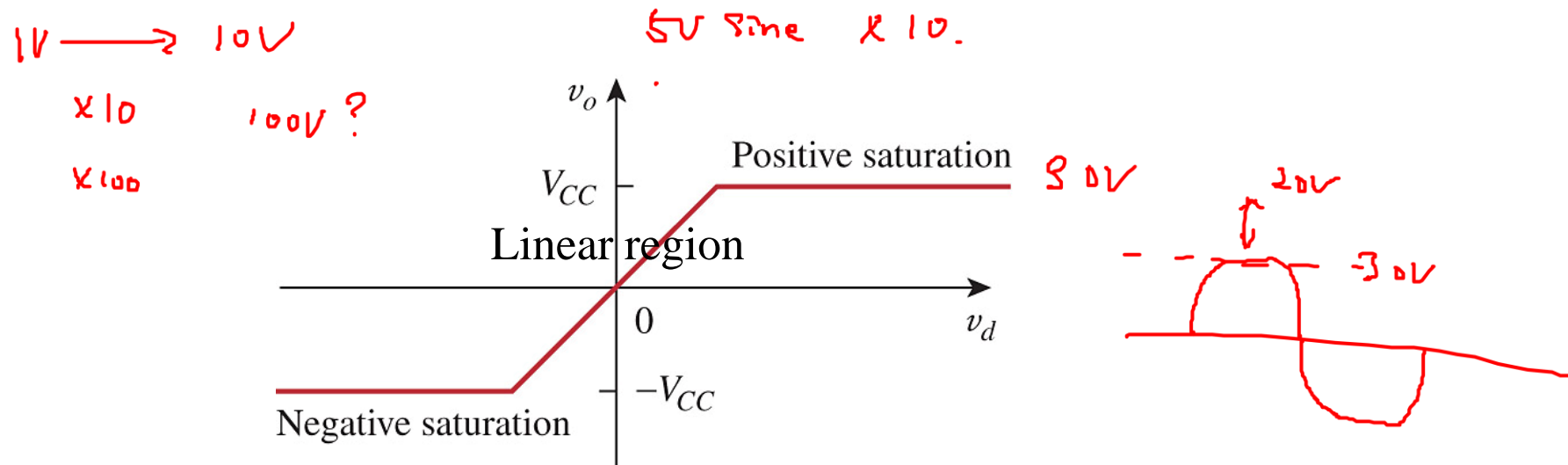

We will assume that our op amps operate in the linear mode

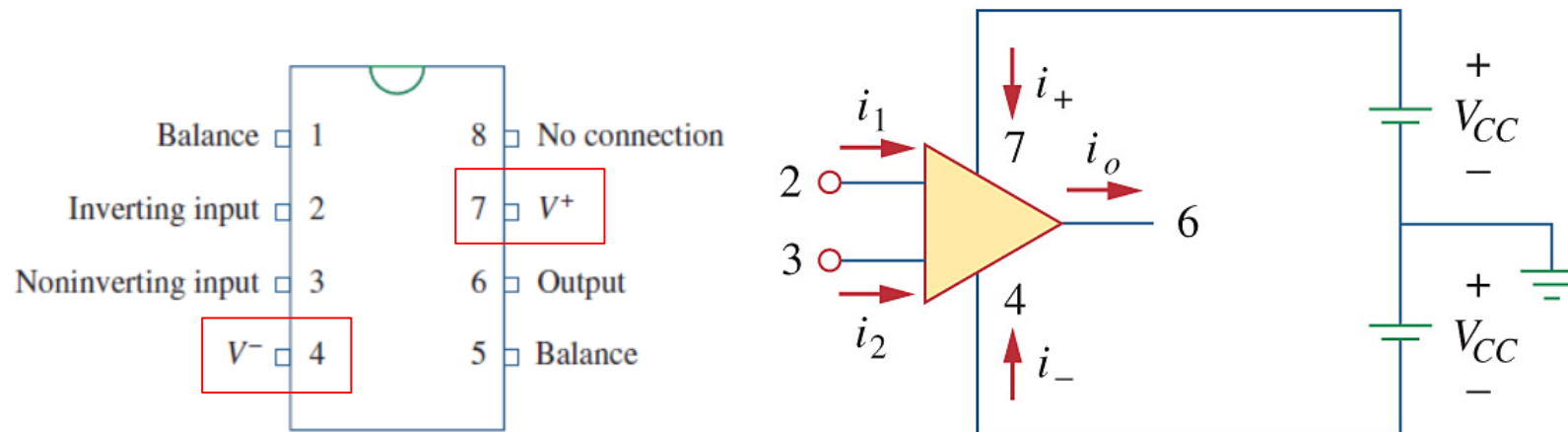
# Powering Op Amp

As an active element, the op amp must be powered by one or two voltage.



Although the power supplies are often ignored in op amp circuit diagrams for the sake of simplicity, the power supply currents must not be overlooked. By KCL,  $i_o = i_1 + i_2 + i_+ + i_-$

# Offset Null

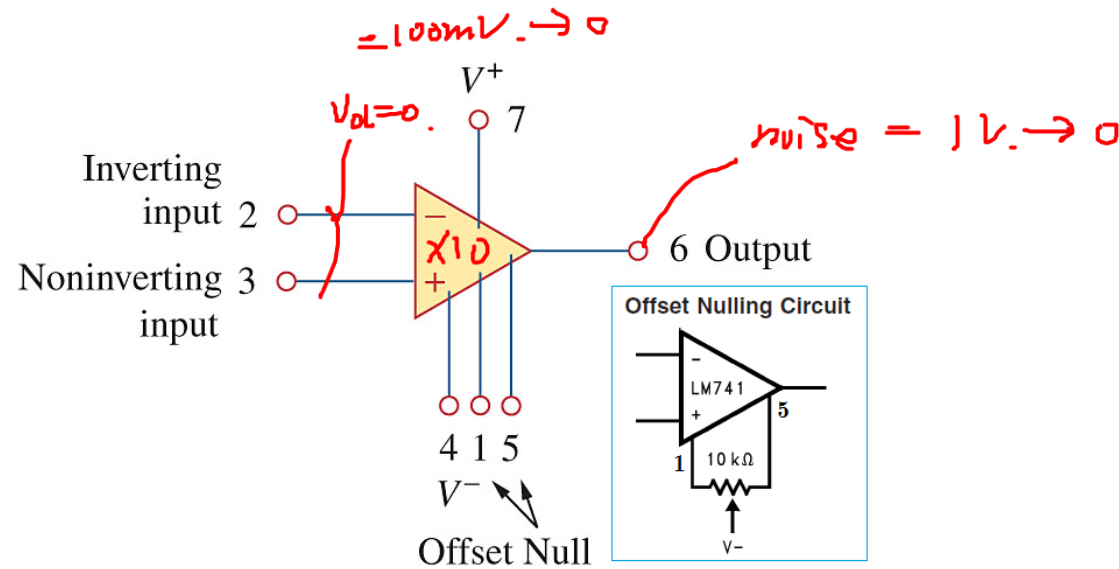

The offset null pin is mainly used to remove the voltage difference between the inverting and non inverting pins.

If there exists some difference in the voltages between two inputs (ideally 0), it will be amplified by the op amp, which will distort output results.


## 5.3 Ideal Op Amp

**Op amp basically amplifies input voltage by the amount of a gain.** From now on we will assume that Op amp is an ideal op amp.

Ideal op amp has the following characteristics:


1. Infinite open-loop gain,  $A = \infty$ .
2. Infinite input resistance,  $R_i = \infty$ .
3. Zero output resistance,  $R_o = 0$ .
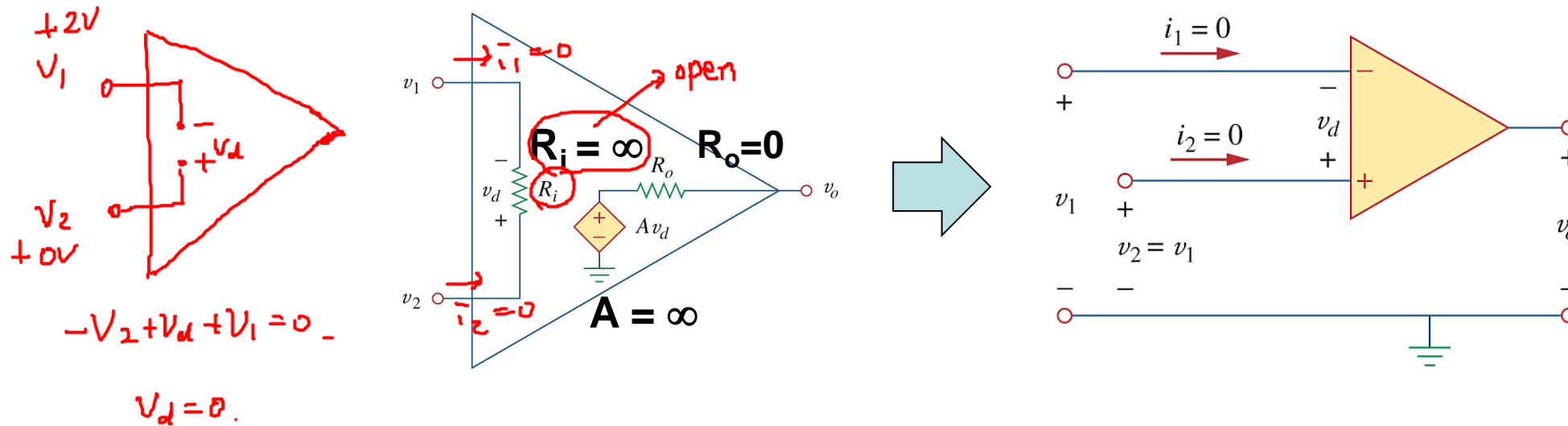
# Important characteristics of ideal op amp




1.  $i_1 = 0$  and  $i_2 = 0$  due to infinite  $R_i \rightarrow$  but the output current is not necessarily zero
2.  $v_1 = v_2$  or  $v_d = v_2 - v_1 = 0 \rightarrow$  **this does not mean  $v_2 = 0$  and  $v_1 = 0$ .**

(i)  $i_1 = i_2 = 0$

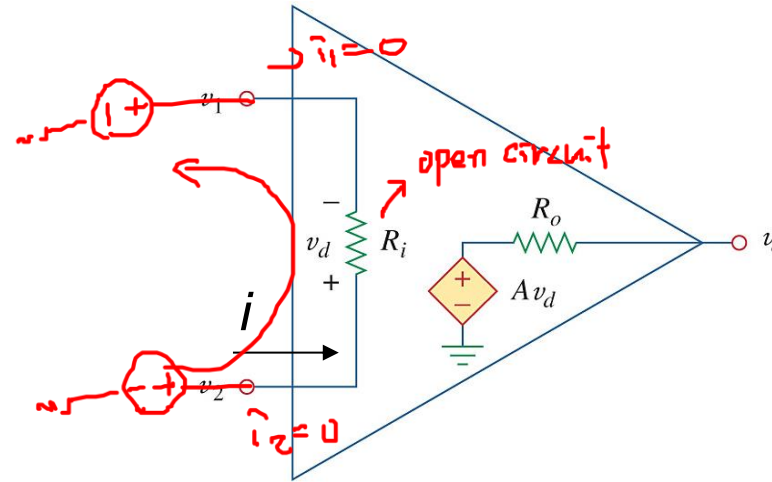


- $R_i$  is infinite  $\rightarrow$  open circuit  $\rightarrow$  no current flows
- By KVL:  $-V_2 + R_i i + V_1 = 0$   $V_1 = V_2$ ,  $V_d = 0$   
because  $R_i$  is infinite  $i = 0 \rightarrow i_1 = i_2 = 0$

(ii)  $v_d = v_2 - v_1 = 0$

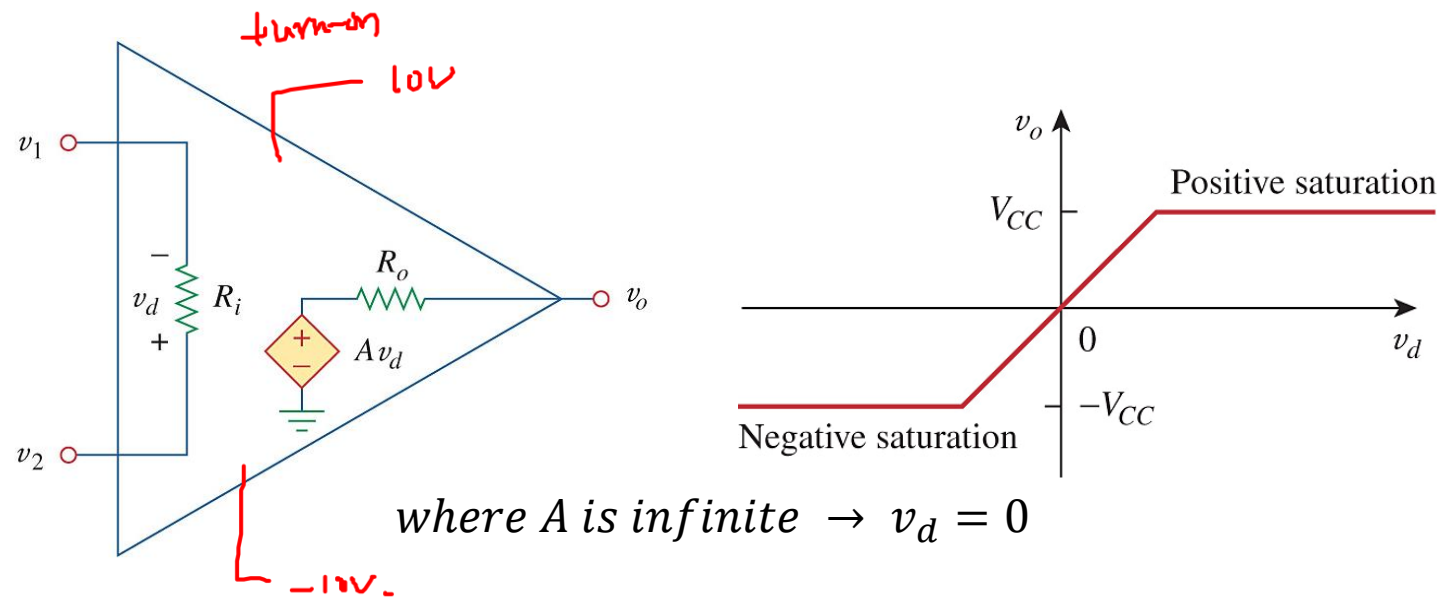

$v_o = \overset{\infty}{A} v_d < \infty$  where  $A$  is infinite  $\rightarrow v_d = 0$

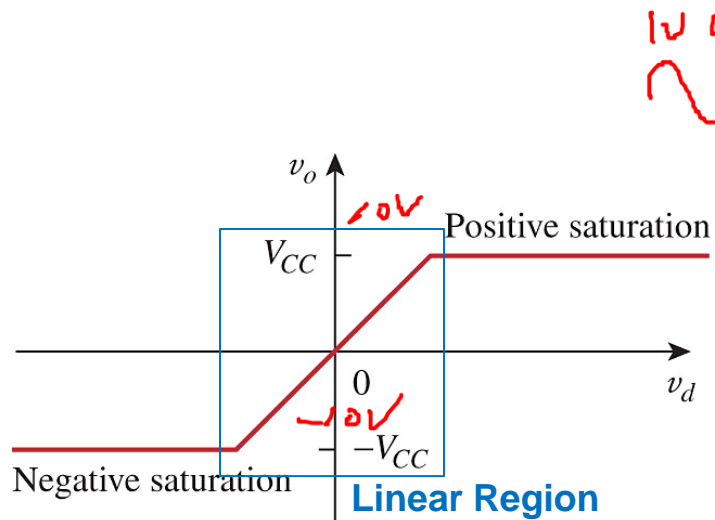Op amp operates in the linear region and therefore  $v_o$  cannot exceed  $V_{CC}$



$$v_o = \begin{cases} -V_{CC} & \text{when } A(v_2 - v_1) < -V_{CC} \\ A(v_2 - v_1) & \text{when } -V_{CC} < A(v_2 - v_1) < +V_{CC} \\ +V_{CC} & \text{when } A(v_2 - v_1) > +V_{CC} \end{cases}$$

When the magnitude of the input voltage difference is small, the op amp behaves **as a linear device**. We use the op amp in the linear operating region, and thus **a constraint is imposed on the input voltages,  $v_1$  and  $v_2$** .


For example,  $V_{CC}$  is 20 V (generally limited to 20 V), and the gain  $A$  is 10,000. In this case, the input voltage difference must be less than 2 mV ( $V_{CC}/A$ ). Because node voltages in the circuits are much larger than 2 mV, a voltage difference of less than 2 mV means the two voltages are essentially equal, i.e.  $v_1 = v_2$ .


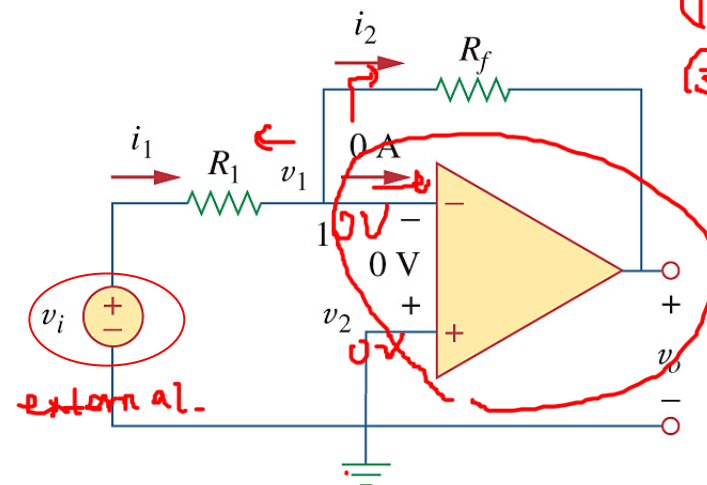
## 5.4 Inverting Amplifier (Inverter)

An inverting amplifier reverses the polarity of the input signal while amplifying it.

The closed-loop gain is  $A_v = \frac{v_o}{v_i} = -\frac{R_f}{R_1}$



①  $V_d = 0$   
②  $i_- = 0$

$$\frac{0 - v_i}{R_1} + \frac{0 - v_o}{R_f} + 0 = 0$$

$$v_o = -\frac{R_f}{R_1} v_i = \text{gain}$$


Input at the inverting terminal

**Proof :**

$$i_1 = i_2 \Rightarrow \frac{v_i - v_1}{R_1} = \frac{v_1 - v_o}{R_f}$$


$$v_1 = v_2 = 0$$
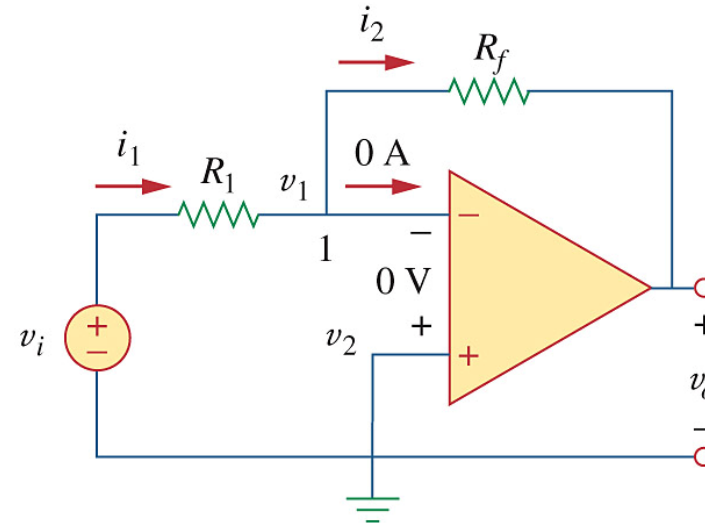
$$\frac{v_i}{R_1} = -\frac{v_o}{R_f} \Rightarrow v_o = -\frac{R_f}{R_1} v_i \Rightarrow A_v = \frac{v_o}{v_i} = -\frac{R_f}{R_1}$$





The gain is the feedback resistance divided by the input resistance  $\rightarrow$  the gain depends only on the external elements connected to the op amp.

# Inverting amplifier equivalent circuit

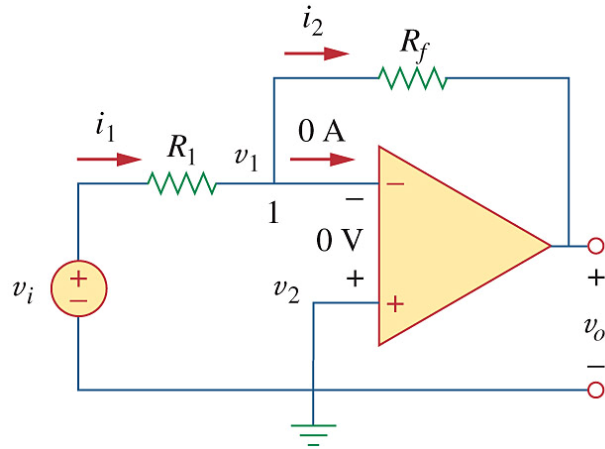

$$v_o = -\frac{R_f}{R_1} v_i$$

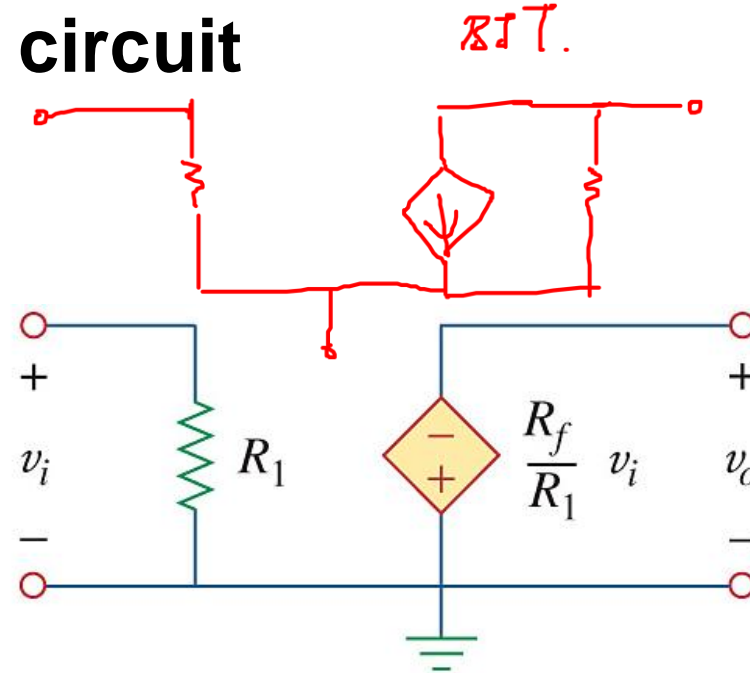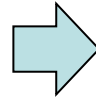

$$v_o = -\frac{R_f}{R_1} v_i$$

**Two circuits are equivalent**

**Example 5.3** Refer to the circuit in Fig.

5.12. If  $v_i = 0.5$  V, calculate (a) the output voltage  $v_o$ , and (b) the current in the 10-k $\Omega$  resistor.

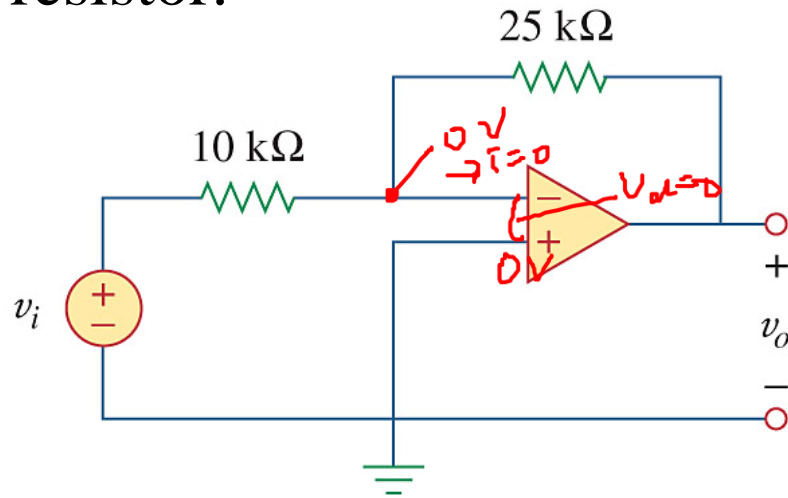


Figure 5.12


$$\frac{0 - v_i}{10k} + \frac{0 - v_o}{25k} = 0$$

Using the equation


$$v_o = -\frac{R_f}{R_1} v_i = -\frac{25}{10} \times 0.5 = -1.25 \text{ (V)}$$

$$i = \frac{v_i}{R_1} = \frac{0.5}{10 \times 10^3} = 5 \times 10^{-5} \text{ (A)} = 50 \text{ } \mu\text{A}$$

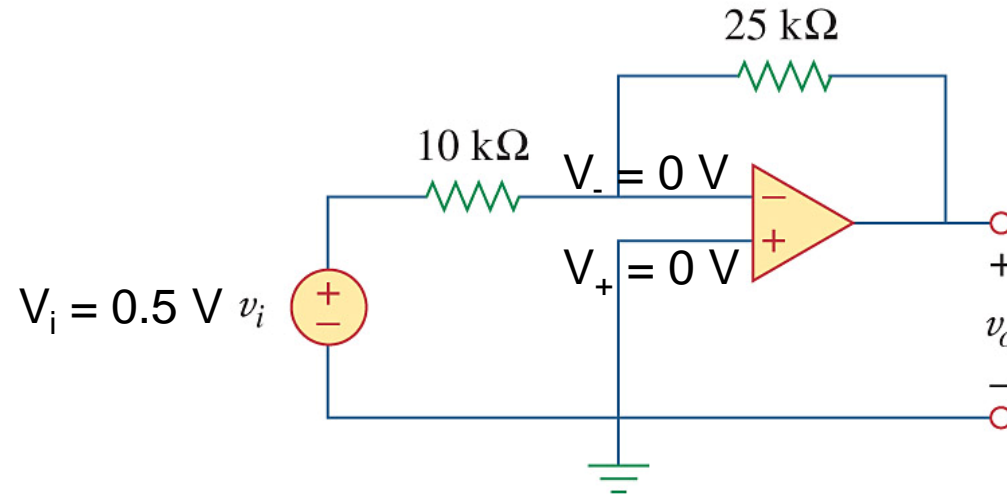What if you do not remember the equation?



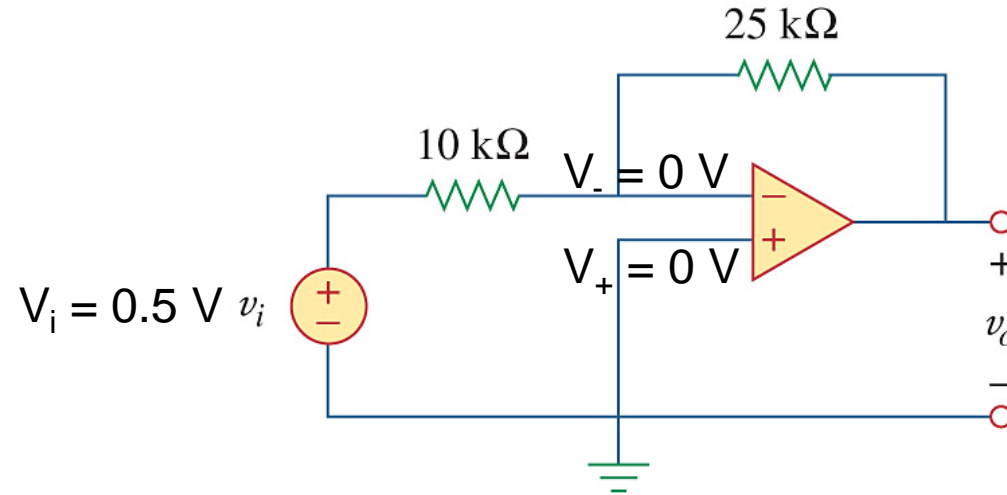What if you do not remember the equation?



$$\frac{0 - 0.5}{10k} + i_- + \frac{0 - v_o}{25k} = 0 \rightarrow -4v_o = 5$$

Therefore  $v_o = -1.25\text{ [V]}$

Current in the  $10\text{ k}\Omega = 0.5/10\text{ k} = 0.5\text{ }\mu\text{A}$

Note: Do not apply KCL at output node (output current is unknown)

## Practical Problem 5.4

Two kinds of current-to-voltage converters (also known as transresistance amplifier) are shown in Fig. 5.15.

(a) Show that for the converter in Fig. 5.15(a),

$$v_o / i_s = -R$$

(b) Show that for the converter in Fig. 5.15(b),

$$v_o / i_s = -R_1(1 + R_3 / R_2 + R_3 / R_1)$$

$R_C, R_L \rightarrow 1^{st}$  ODE  
 $RLC \rightarrow 2^{nd}$  ODE

$$\textcircled{1} -\bar{i}_s + \frac{0 - v_a}{R_1} = 0 \quad v_a = -R_1 \bar{i}_s$$

$$\textcircled{2} \frac{v_a - 0}{R_1} + \frac{v_a - v_o}{R_3} + \frac{v_a - 0}{R_2} = 0$$


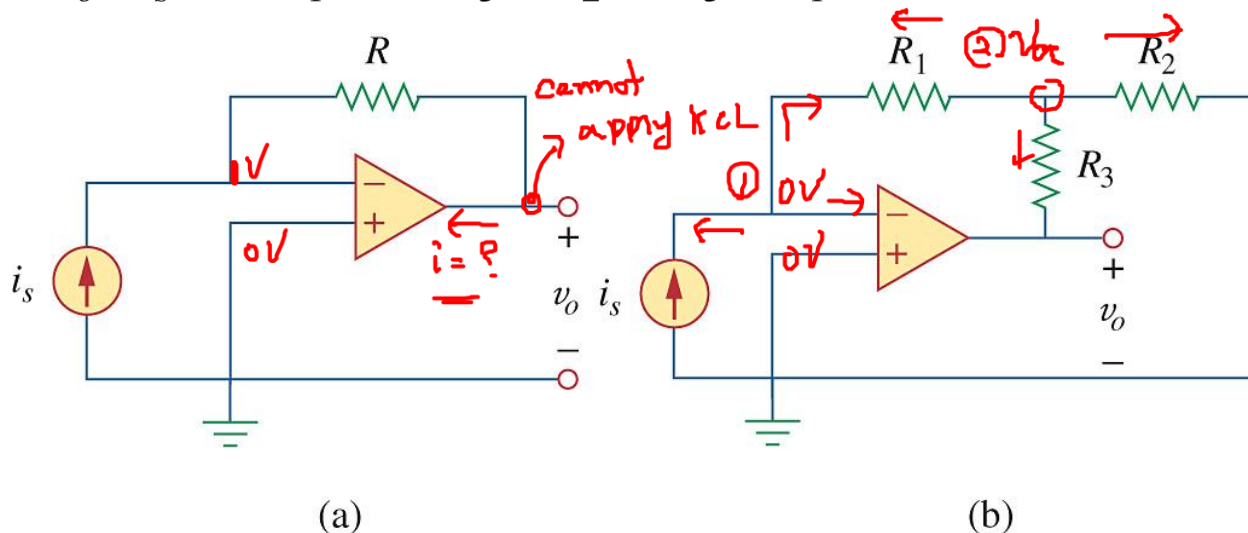


Figure 5.15

(a)

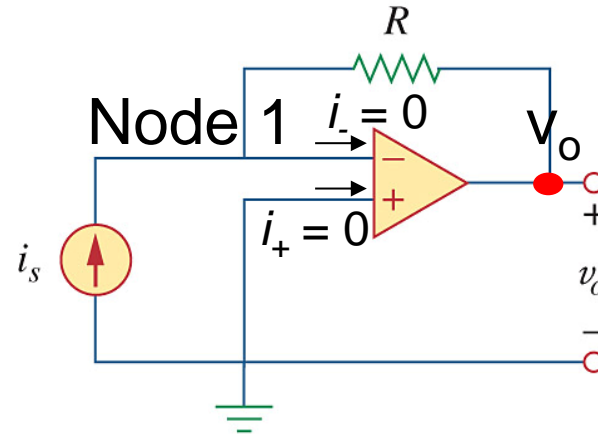

(i)  $V_+ = 0$  because it is grounded

(ii) Therefore,  $V_- = 0$


Nodal analysis from the Node 1 ( $V = 0$ )

$$-i_s + i_- + \frac{0 - v_o}{R} = 0 \text{ where } i_- = 0$$

$$i_s = \frac{-v_o}{R} \rightarrow \frac{v_o}{i_s} = -R$$



(b)

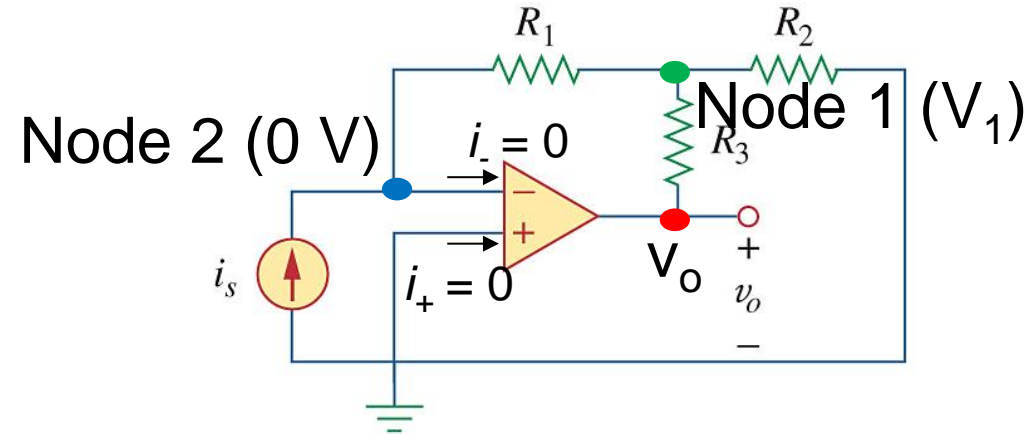

(i)  $V_+ = 0$  because it is grounded


(ii) Therefore,  $V_- = 0$

Nodal analysis from the Node 1 ( $V_1$ ) and Node 2 (0 V)

$$\frac{V_1 - 0}{R_1} + \frac{V_1 - v_o}{R_3} + \frac{V_1 - 0}{R_2} = 0$$

$$-i_s + i_- + \frac{0 - V_1}{R_1} = 0 \rightarrow -i_s R_1 = V_1 \text{ (put into the first eq.)}$$

(b)

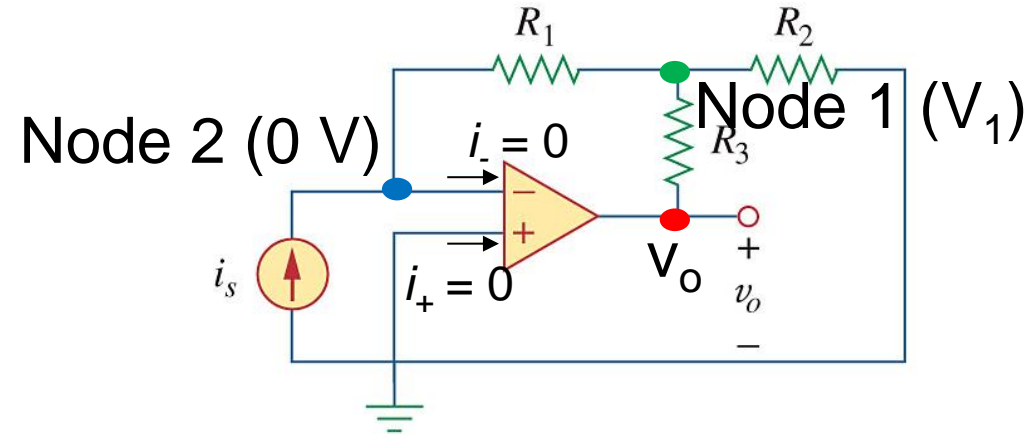

$$\frac{-i_s R_1 - 0}{R_1} + \frac{-i_s R_1 - v_o}{R_3} + \frac{-i_s R_1 - 0}{R_2} = 0$$
$$-i_s(R_1 R_2 + R_1 R_3 + R_2 R_3) = R_2 v_o$$

$$\frac{v_o}{i_s} = -\frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2}$$

$$= -R_1 \left( 1 + \frac{R_3}{R_2} + \frac{R_3}{R_1} \right)$$

## 5.5 Noninverting Amplifier

Noninverting amplifier circuit: the input  $v_i$  is applied directly at the noninverting input terminal. This provides **positive voltage gain**.


$$\frac{v_i - 0}{R_1} + \frac{v_i - v_o}{R_f} + i_- = 0 \quad \text{① } i_- = 0$$

$$\text{② } v_i = v_+$$


The closed-loop gain is

$$A_v = \frac{v_o}{v_i} = 1 + \frac{R_f}{R_1}$$
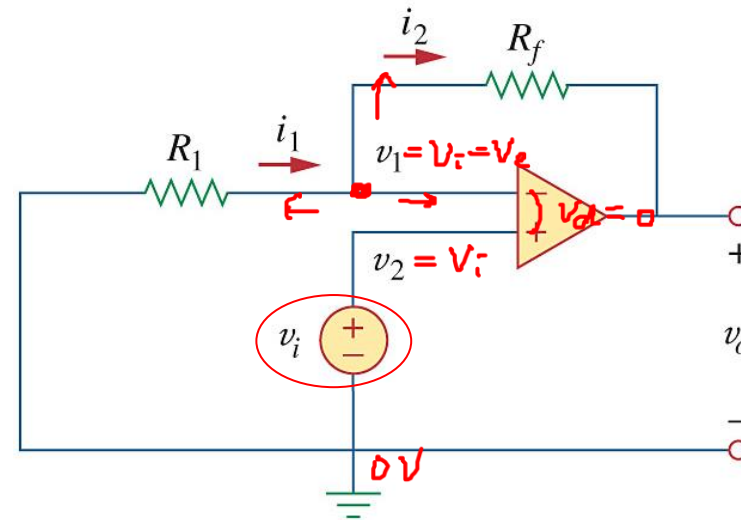
$$v_o = \left(1 + \frac{R_f}{R_1}\right)v_i$$



Input at the noninverting terminal

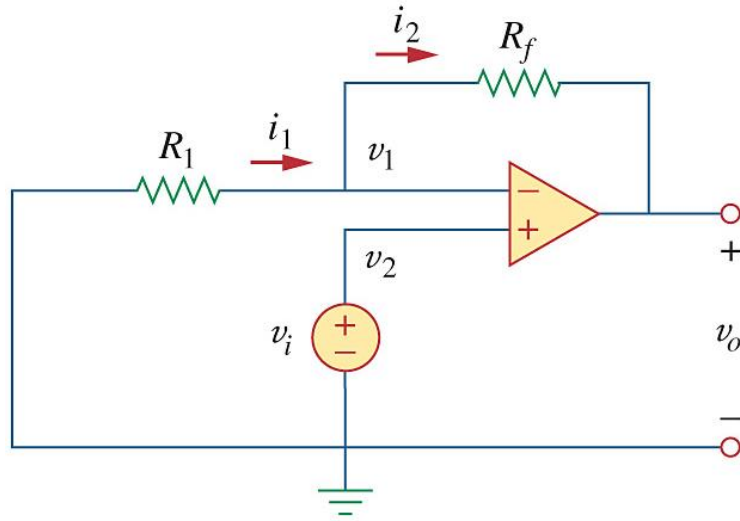

**Proof :**


$$i_1 = i_2 \Rightarrow \frac{0 - v_1}{R_1} = \frac{v_1 - v_o}{R_f} \Rightarrow \frac{v_o}{v_1} = 1 + \frac{R_f}{R_1}$$

$$v_1 = v_2 = v_i$$

$$A_v = \frac{v_o}{v_i} = 1 + \frac{R_f}{R_1}$$

Again, the gain depends only on the external resistors


# Voltage follower circuit

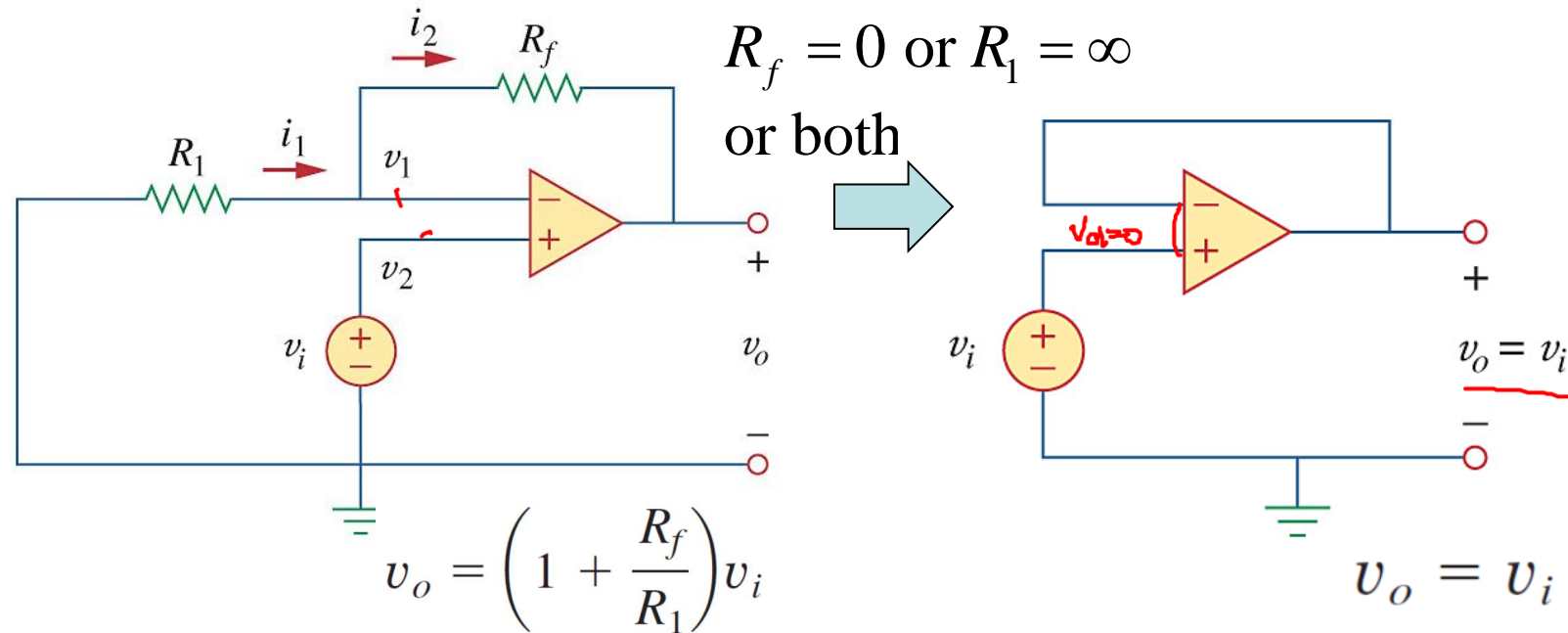

When  $R_f = 0$  or  $R_1 = \infty$  or both, then the gain is 1, which means  $\mathbf{v_i = v_o} \rightarrow \mathbf{voltage\ follower}$

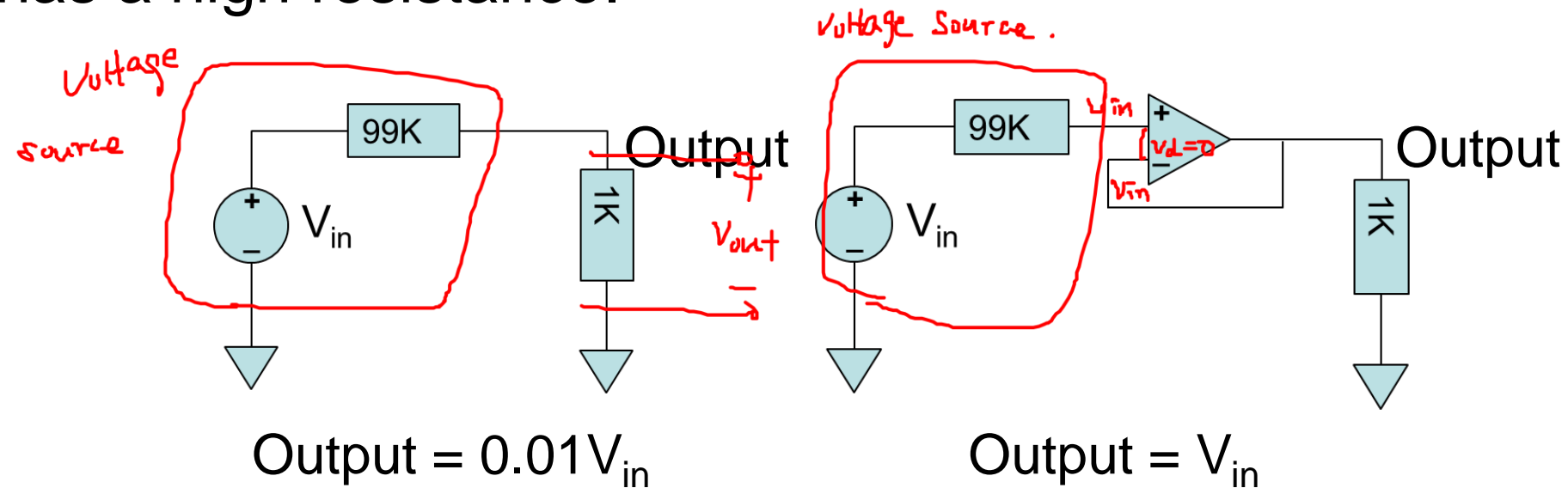
## Voltage follower circuit

**Advantage:** It can supply a large current at the output while drawing almost no current from the input when the source has a high resistance.



Although the voltage gain is only 1, the power gain is much larger.

# Negative Feedback

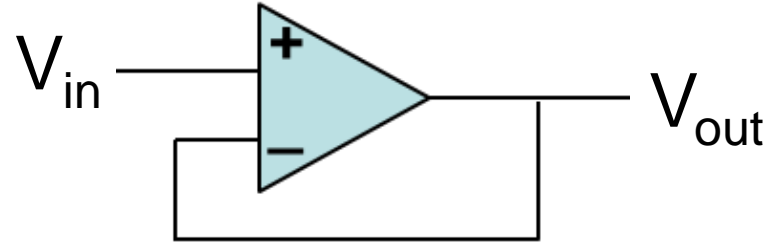


**Negative feedback** is when the occurrence of an event causes something to happen that counteracts the original event.

If op amp output  $V_{out}$  falls then  $V_-$  will fall by the same amount, and thus,  $(V_+ - V_-)$  will increase. **Negative feedback adjusts the output to make  $V_+ \cong V_-$**

$$V_{out} \downarrow = AV_d = A(V_+ - V_- \downarrow) = A(\overbrace{V_{in} - V_{out} \downarrow}^{V_d \uparrow}) \rightarrow V_{out} \uparrow$$

$$V_{out}(1 + A) = AV_{in} \rightarrow V_{out} = \frac{1}{1 + 1/A} V_{in} \rightarrow V_{in} \text{ for large } A$$

# Voltage follower circuit as a buffer

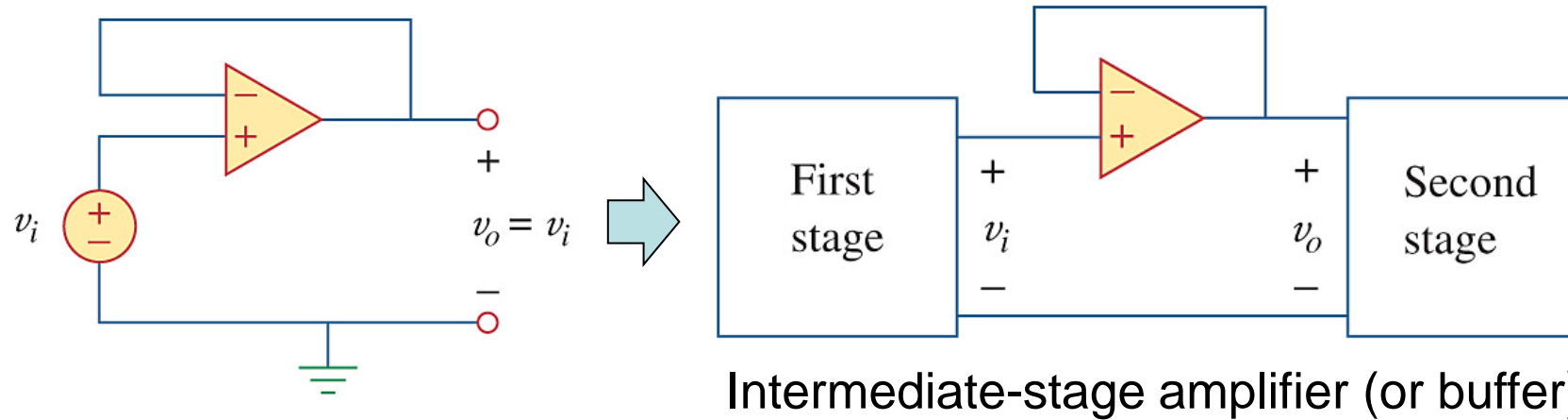

Due to **very high input impedance**, the voltage follower circuit is useful as an intermediate-stage (or **buffer**) amplifier to isolate one circuit from another.

→ minimizes interaction between the two stages and eliminates interstage loading.




## 5.6 Summing Amplifier (Adder)

The op amp also can perform addition and subtraction.

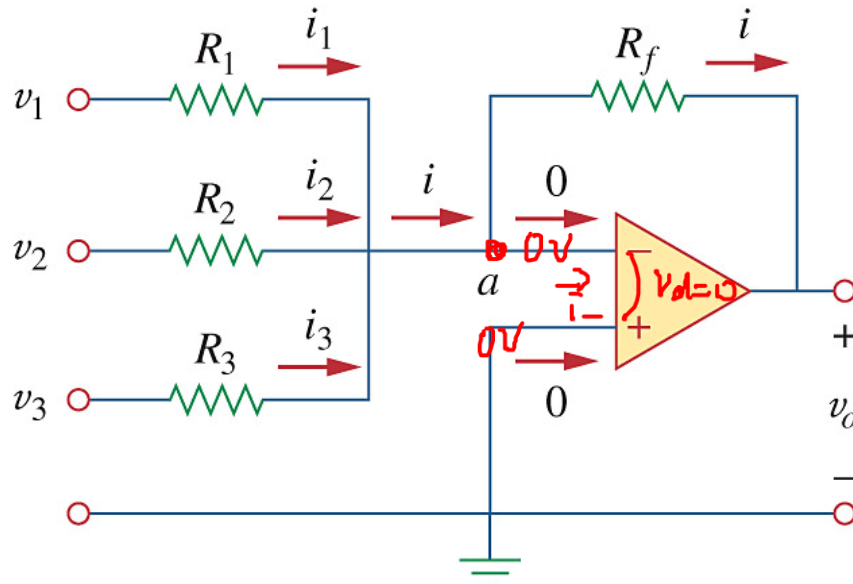**A summing amplifier** is an op amp circuit that combines several inputs and produces **an output that is the weighted sum of the inputs.**

$$\frac{0 - v_1}{R_1} + \frac{0 - v_2}{R_2} + \frac{0 - v_3}{R_3} + \frac{0 - v_o}{R_f} + \cancel{i} = 0$$



$$v_o = - \left( \frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3 \right)$$


All inputs at the inverting terminal


**Proof :**

$$i = i_1 + i_2 + i_3 \Rightarrow$$

$$\frac{0 - v_o}{R_f} = \frac{v_1 - 0}{R_1} + \frac{v_2 - 0}{R_2} + \frac{v_3 - 0}{R_3}$$
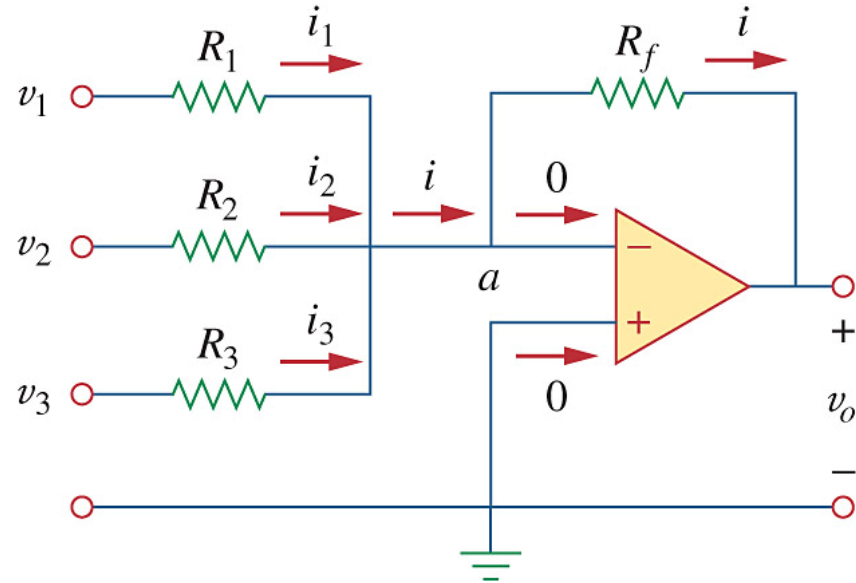
$$v_o = - \left( \frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3 \right)$$



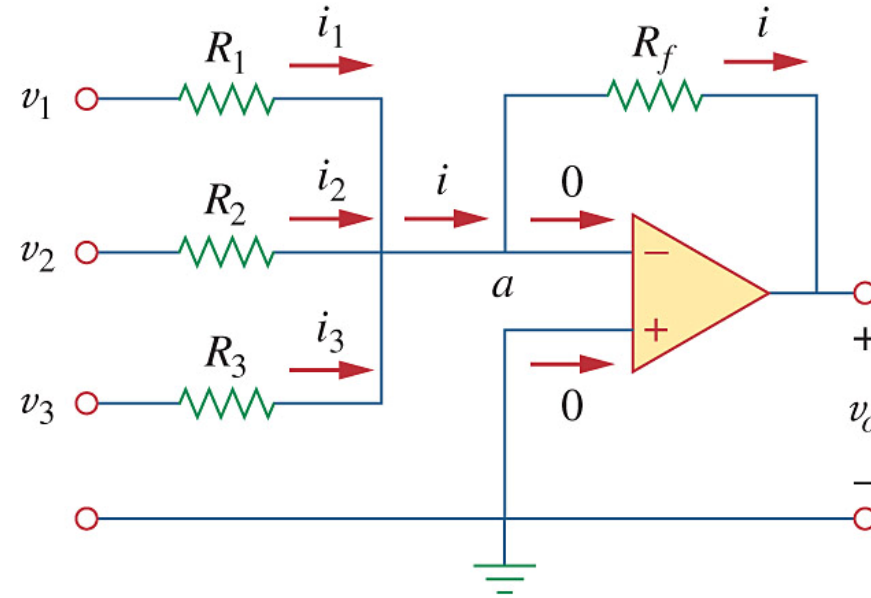


If  $R_3 = R_2 = R_1$ , then

$$v_o = -\frac{R_f}{R_1} (v_1 + v_2 + v_3)$$

If  $R_3 = R_2 = R_1 = R_f$ , then

$$v_o = -(v_1 + v_2 + v_3)$$

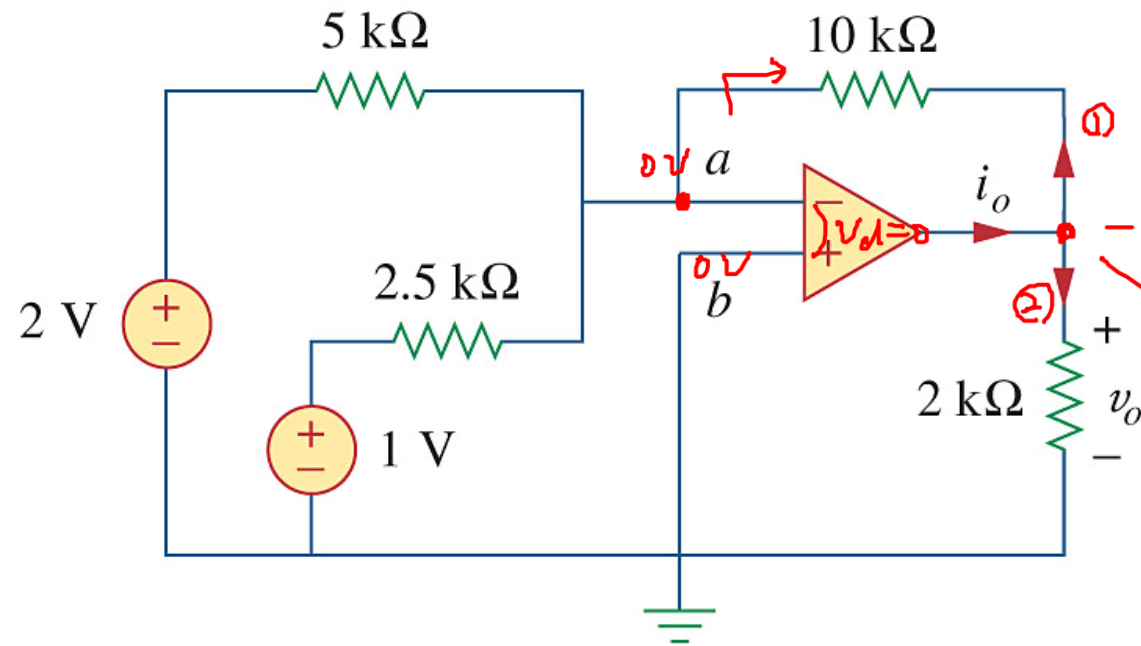
**Example 5.6** Calculate  $v_o$  and  $i_o$  in the op amp circuit in Fig. 5.22.



$$\frac{0-2}{5\text{K}} + \frac{0-1}{2.5\text{K}} + \frac{0-v_o}{10\text{K}} + \frac{v_o}{2\text{K}} = 0$$

$$v_o = -8\text{ V}$$

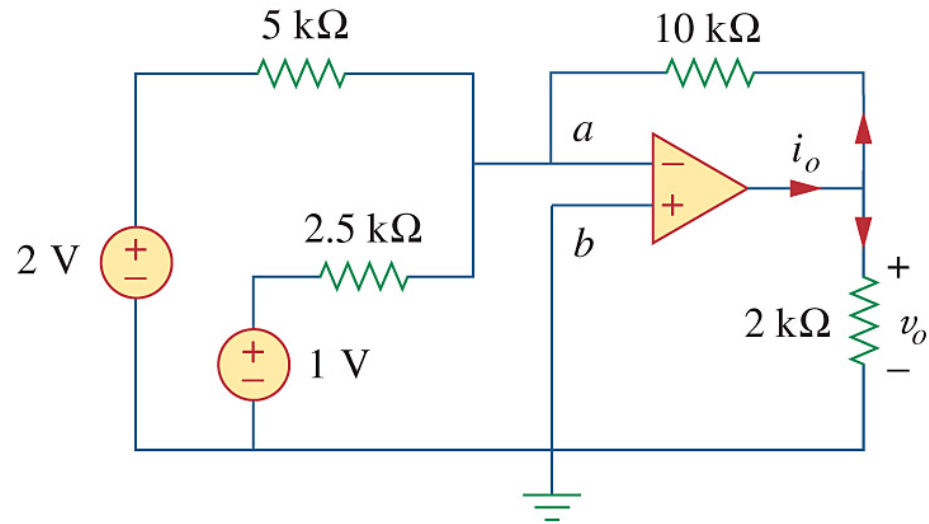by KCL:  $i_o = \textcircled{1} + \textcircled{2}$




$$v_o = -\left(\frac{R_f}{R_1}v_1 + \frac{R_f}{R_2}v_2\right) = -\frac{10k}{5k}2 - \frac{10k}{2.5k}1 = -8\text{ V}$$

$$i_o = \frac{v_o}{2k} + \frac{v_o - 0}{10k} = \frac{-8}{2k} + \frac{-8}{10k} = -0.0048\text{ A} = -4.8\text{ mA}$$
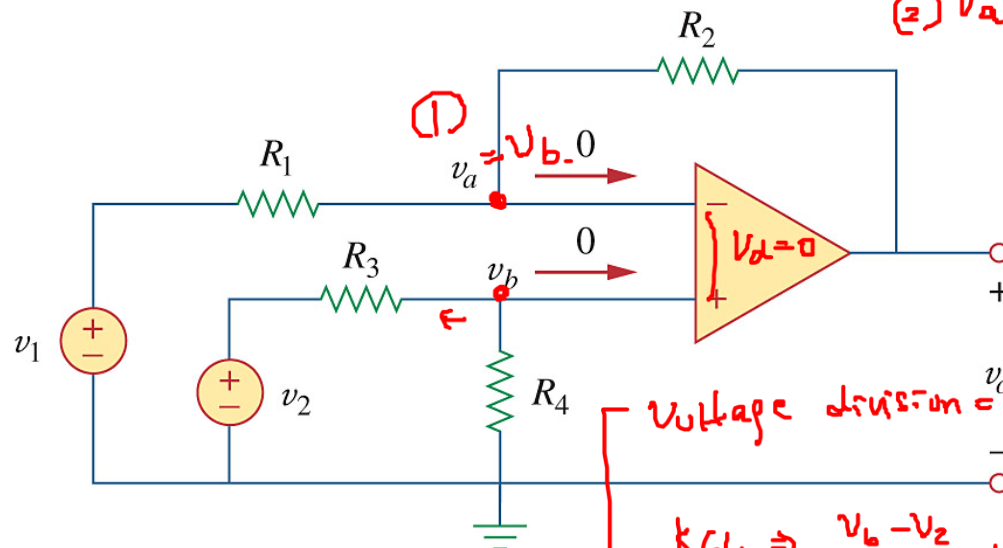
## 5.7 Difference Amplifier (Subtractor)

**Difference (or differential) amplifiers** are used in various applications where there is a need to **amplify the difference between two input signals**.



$$v_o = \left( \frac{R_2}{R_1} + 1 \right) \frac{R_4}{R_3 + R_4} v_2 - \frac{R_2}{R_1} v_1$$


$$v_o = \frac{R_2(1 + R_1/R_2)}{R_1(1 + R_3/R_4)} v_2 - \frac{R_2}{R_1} v_1$$

Handwritten note: Voltage division  $= \frac{R_4}{R_3 + R_4} v_2 = v_b$

Handwritten note: KCL  $\Rightarrow \frac{v_b - v_2}{R_3} + \frac{v_b}{R_4} + i_4 = 0$

Inputs at both inverting and noninverting terminal

# Proof

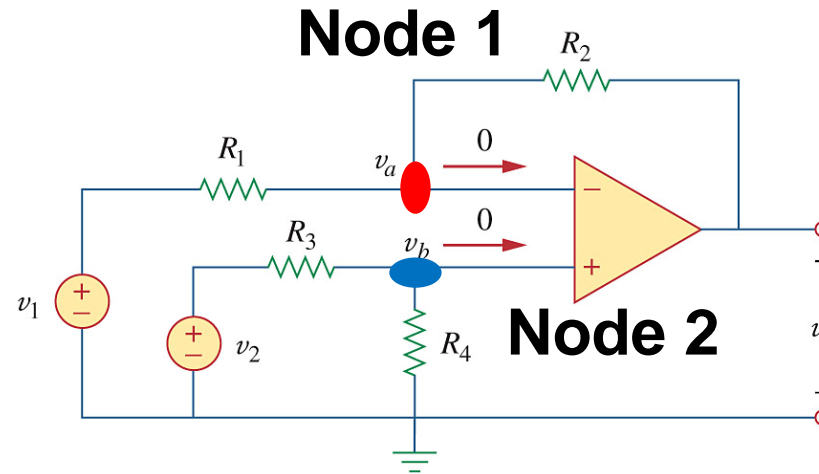

**Node 1:**

$$\frac{v_a - v_1}{R_1} + \frac{v_a - v_o}{R_2} = 0 \rightarrow R_2 \left( \frac{1}{R_1} + \frac{1}{R_2} \right) v_a - \frac{R_2}{R_1} v_1 = v_o$$

**Node 2:**

$$\frac{v_b - v_2}{R_3} + \frac{v_b - 0}{R_4} = 0, \text{ because } v_a = v_b$$
$$v_a = v_b = \frac{R_4}{R_3 + R_4} v_2$$

Put into the equation

$$R_2 \left( \frac{1}{R_1} + \frac{1}{R_2} \right) \textcircled{v_a} - \frac{R_2}{R_1} v_1 = v_o \quad \textcircled{v_a} = v_b = \frac{R_4}{R_3 + R_4} v_2$$

$$\rightarrow \left( 1 + \frac{R_2}{R_1} \right) \left( \frac{R_4}{R_3 + R_4} \right) v_2 - \frac{R_2}{R_1} v_1 = v_o$$

$$v_o = \frac{R_2(1 + R_1/R_2)}{R_1(1 + R_3/R_4)} v_2 - \frac{R_2}{R_1} v_1$$



Because a difference amplifier must reject a signal common to the two inputs, the amplifier must have the property that  $v_o = 0$  when  $v_1 = v_2$ .


$$v_o = \frac{R_2(1 + R_1/R_2)}{R_1(1 + R_3/R_4)}v_2 - \frac{R_2}{R_1}v_1$$

If  $R_4 / R_3 = R_2 / R_1$ , then

$$v_o = \frac{R_2}{R_1}(v_2 - v_1)$$


If  $R_2 = R_1$  and  $R_3 = R_4$  then

$$v_o = v_2 - v_1 \quad \text{red } -0$$

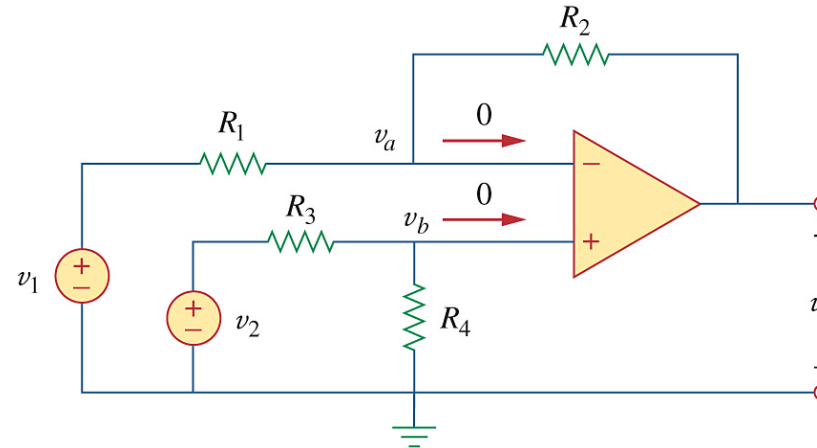

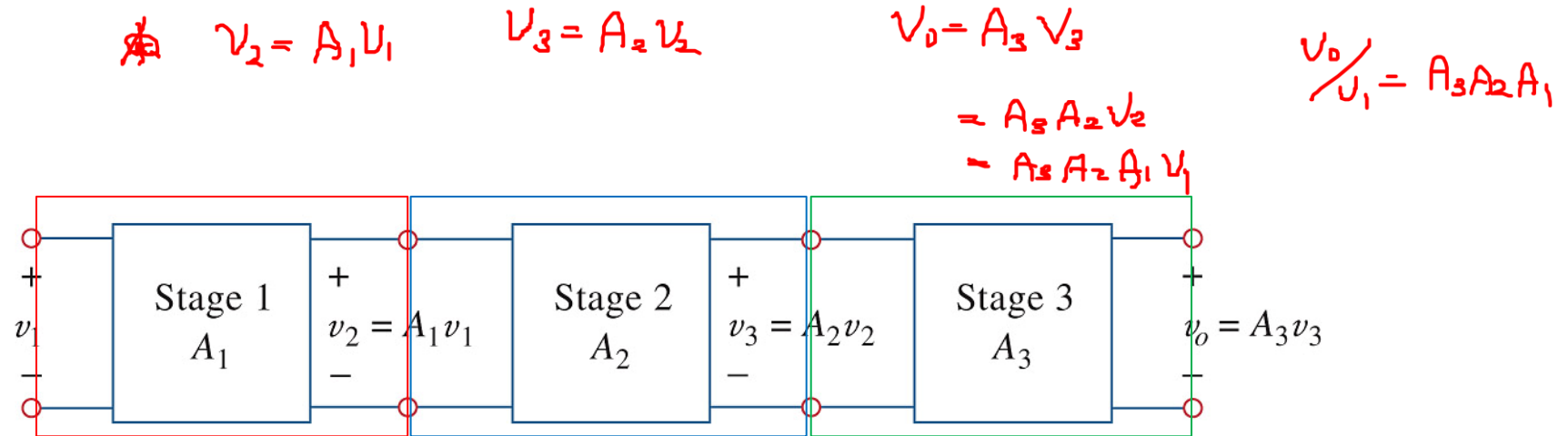
## 5.8 Cascaded Op Amp Circuits

A cascade connection is a head-to-tail arrangement of several op amp circuits such that **the output of one is the input of the next.**



Each circuit is called Stage


## Gain of Cascaded Op Amp

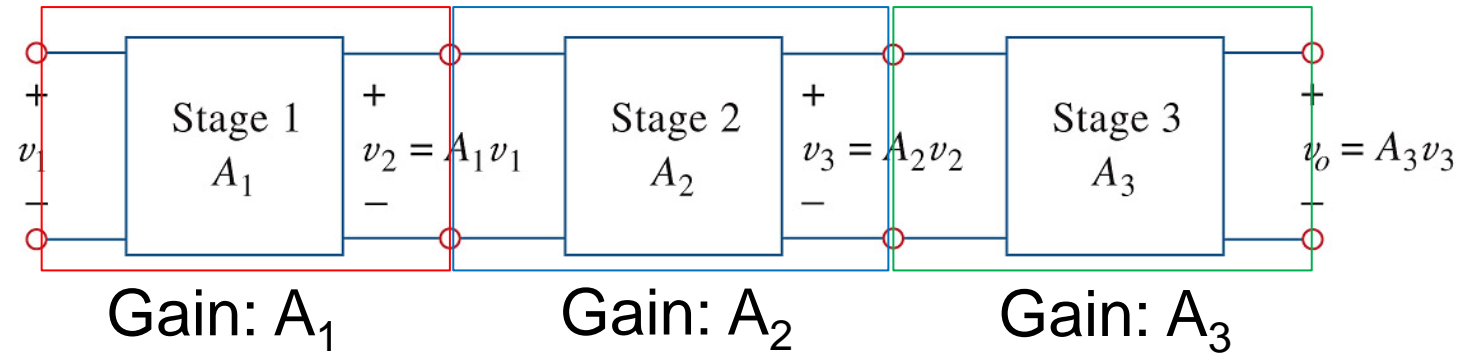

Original input signal is increased by the **gain of the individual stage**, and the final gain is **the product of all gains at each stage**.

$$A = \frac{v_o}{v_1} = \frac{v_2}{v_1} \cdot \frac{v_3}{v_2} \cdot \frac{v_o}{v_3} = A_1 A_2 A_3$$

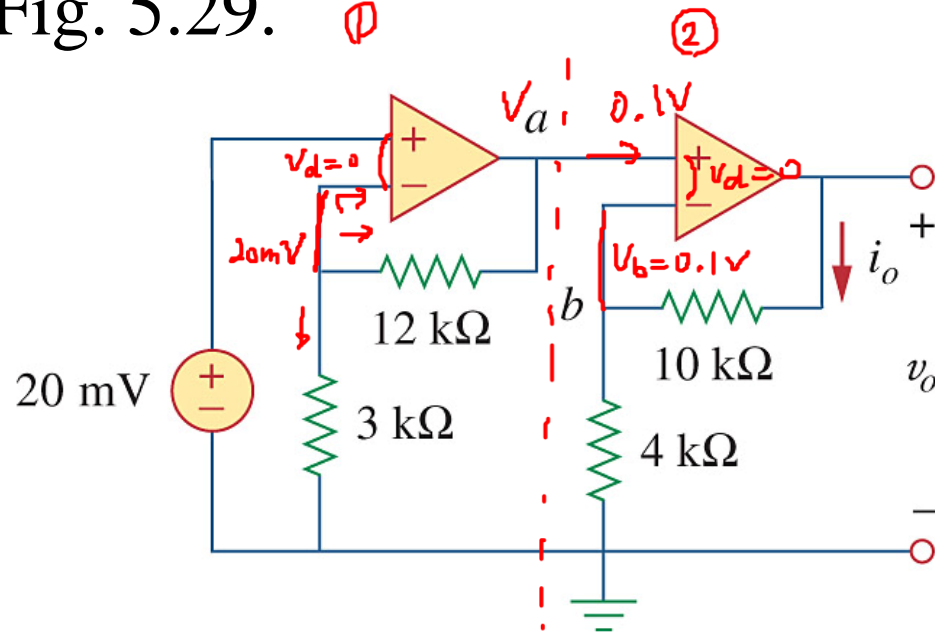**Example 5.9** Find  $v_o$  and  $i_o$  in the circuit in Fig. 5.29.




$$\textcircled{1} \quad \frac{20\text{mV} - 0}{3\text{k}} + \frac{20\text{mV} - V_a}{12\text{k}} + i = 0$$

$$V_a = 0.1\text{V}$$

$$\textcircled{2} \quad \frac{0.1 - 0}{4\text{k}} + \frac{0.1 - V_o}{10\text{k}} + i = 0$$

$$V_o = 0.35\text{V}$$

$$i_o = \frac{0.35 - 0.1}{10\text{k}}$$

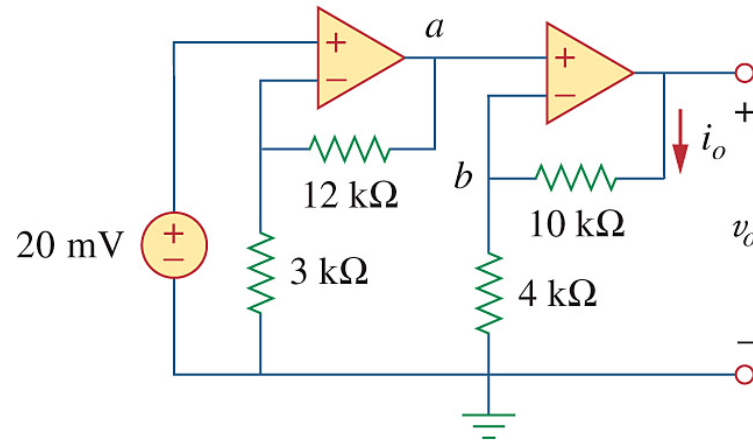


Input is to  $V_+$   $\rightarrow$  noninverting amplifier  $A_v = \frac{v_o}{v_i} = 1 + \frac{R_f}{R_1}$

$$v_a = \left(1 + \frac{12}{3}\right) \times 20 \times 10^{-3} = 0.1 \text{ (V)}$$

$$v_o = \left(1 + \frac{10}{4}\right) v_a = \left(1 + \frac{10}{4}\right) \times 0.1 = 0.35 \text{ (V)}$$
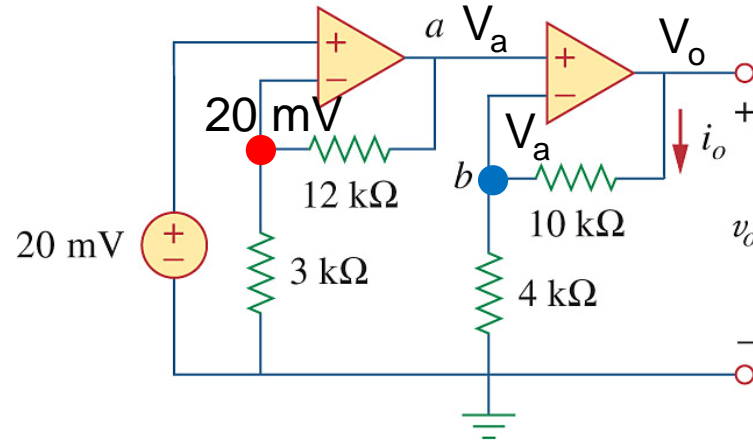
$$i_o = \frac{v_o}{10 + 4} = \frac{0.35}{14} = 0.025 \text{ (mA)} = 25 \text{ } \mu\text{A}$$



I don't remember any equation.. then,

(1) First op amp

$$\text{By KCL: } \frac{20\text{mV} - V_a}{12k} + \frac{20\text{mV}}{3k} = 0 \rightarrow V_a = 0.1 \text{ V}$$

(2) Second op amp

$$\text{By KCL: } \frac{0.1 - V_o}{10k} + \frac{0.1}{4k} = 0 \rightarrow V_o = 0.35 \text{ V}$$

$$i_o = V_o/14k = 0.025 \text{ mA} = 25 \text{ } \mu\text{A}$$

**Example 5.10** If  $v_1 = 1$  V and  $v_2 = 2$  V, find  $v_o$  in the op amp circuit of Fig. 5.31.

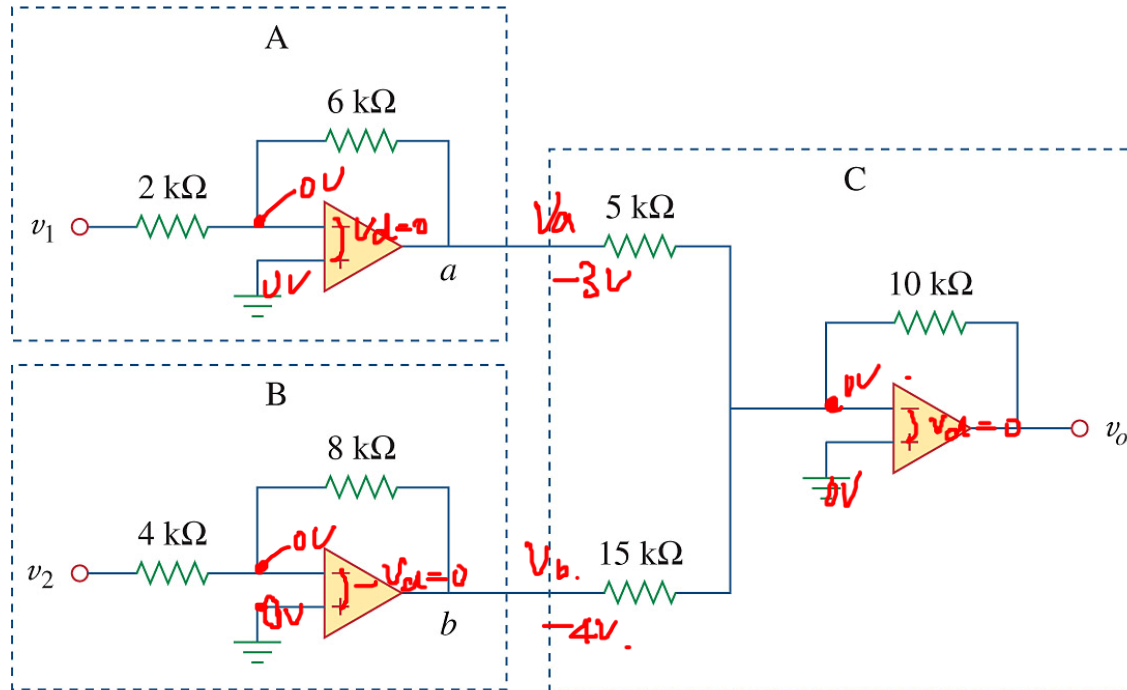


Figure 5.31

$$A: \frac{0 - v_1}{2k} + \frac{0 - v_a}{6k} + i = 0$$

$$v_1 = 1 \text{ V}$$

$$v_a = -3 \text{ V}$$


$$B: \frac{0 - v_2}{4k} + \frac{0 - v_b}{8k} + i = 0$$

$$v_2 = 2 \text{ V}$$

$$v_b = -4 \text{ V}$$

$$C: \frac{0 - (-3)}{5k} + \frac{0 - (-4)}{15k} + \frac{0 - v_o}{10k} + i = 0$$


$$v_o = 0.67 \text{ V}$$

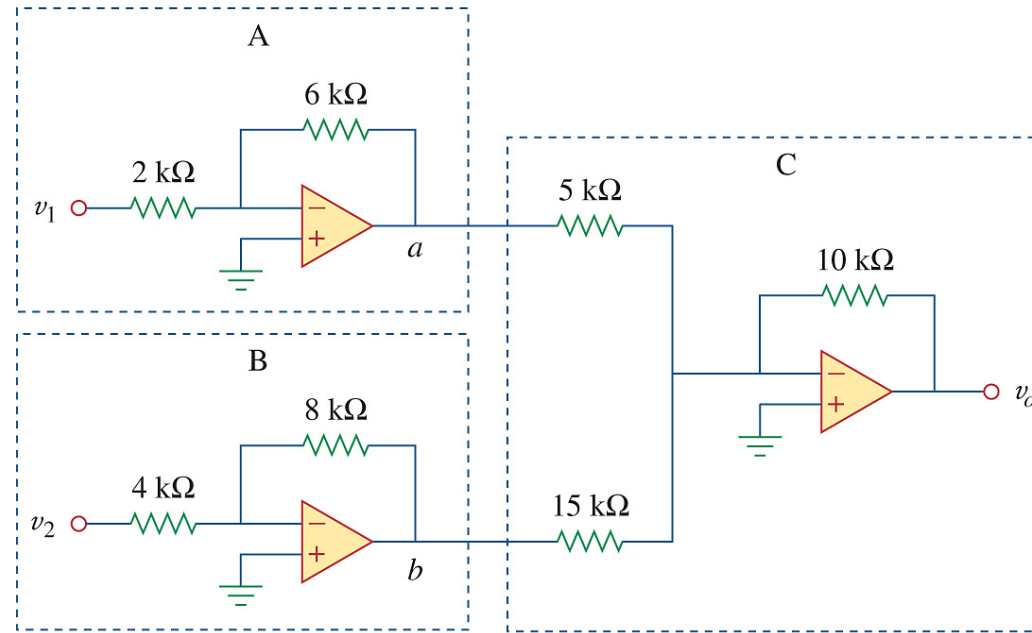

We have this scary circuit.. Take a look at **each stage**

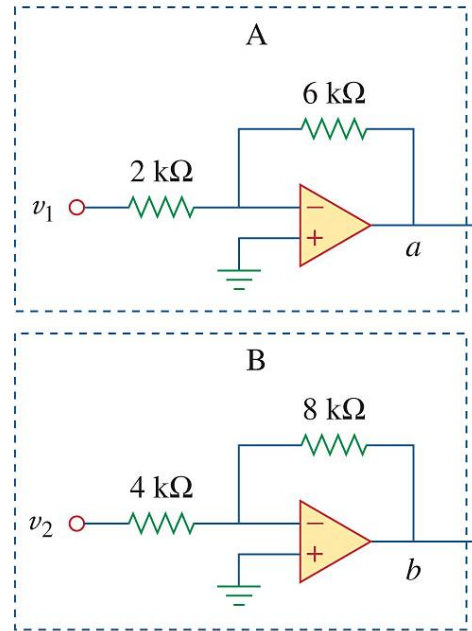- A and B are noninverting amplifiers.
- C is a summing amplifier.
- Solve it stage by stage.






$$v_o = -\frac{R_f}{R_1} v_i$$

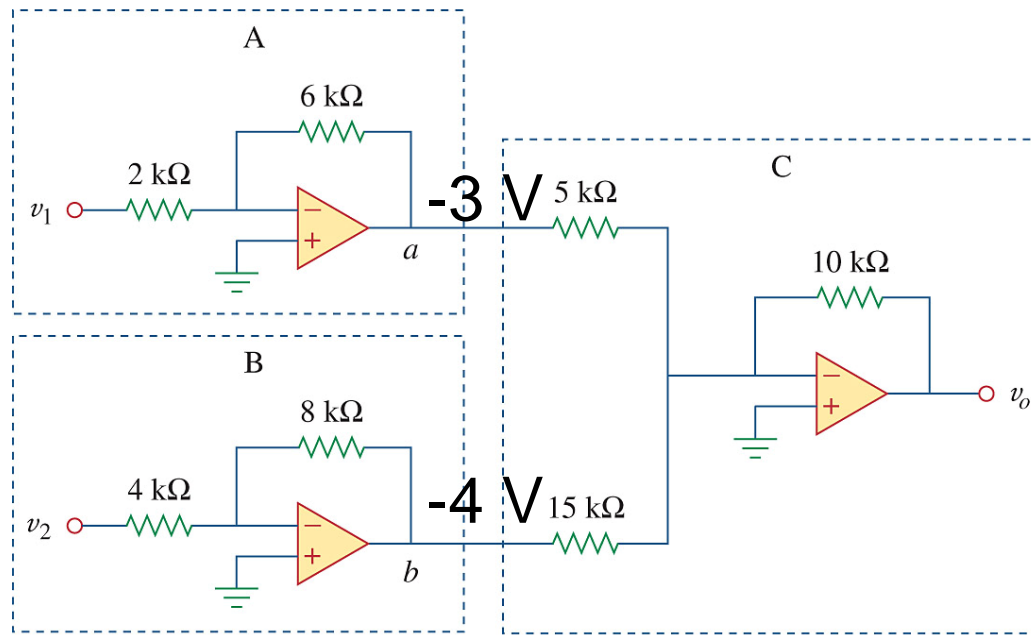**A and B are inverting amplifiers**

$$v_a = -\frac{6}{2} v_1 = -\frac{6}{2} \times 1 = -3 \text{ (V)}$$

$$v_b = -\frac{8}{4} v_2 = -\frac{8}{4} \times 2 = -4 \text{ (V)}$$



**C is a summing amplifier**

$$v_o = -\left(\frac{R_f}{R_1}v_1 + \frac{R_f}{R_2}v_2 + \frac{R_f}{R_3}v_3\right)$$

$$v_o = -\left(\frac{10}{5}v_a + \frac{10}{15}v_b\right)$$

$$= -\left(\frac{10}{5} \times (-3) + \frac{10}{15} \times (-4)\right) = \frac{26}{3} \approx 8.67 \text{ (V)}$$


**Again, you can solve it by using KCL without using equations**

## 5.10. Applications


- The op amp is a fundamental building block in modern electronic instrumentation.
- e.g. digital-to-analog converters, analog computers, etc.  
DAC.
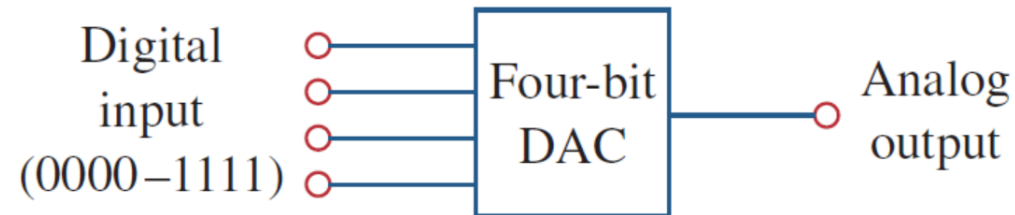
# Digital-to-Analog Converter

- The digital-to-analog converter (DAC) transforms digital signals into analog form.
- Example: a four-bit DAC




# DAC: binary weighted ladder

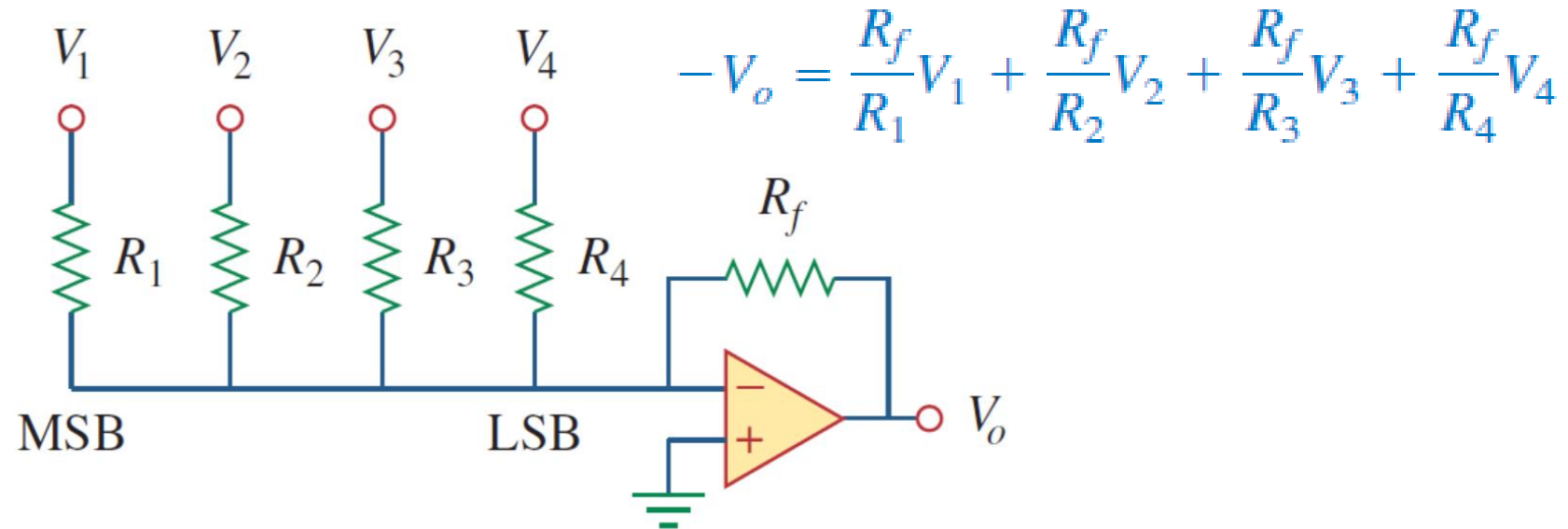


- An inverting summing amplifier
- Bits are weighted by descending value of  $R_f/R_n$  to produce 2 times difference for adjacent bits

# DAC: binary weighted ladder

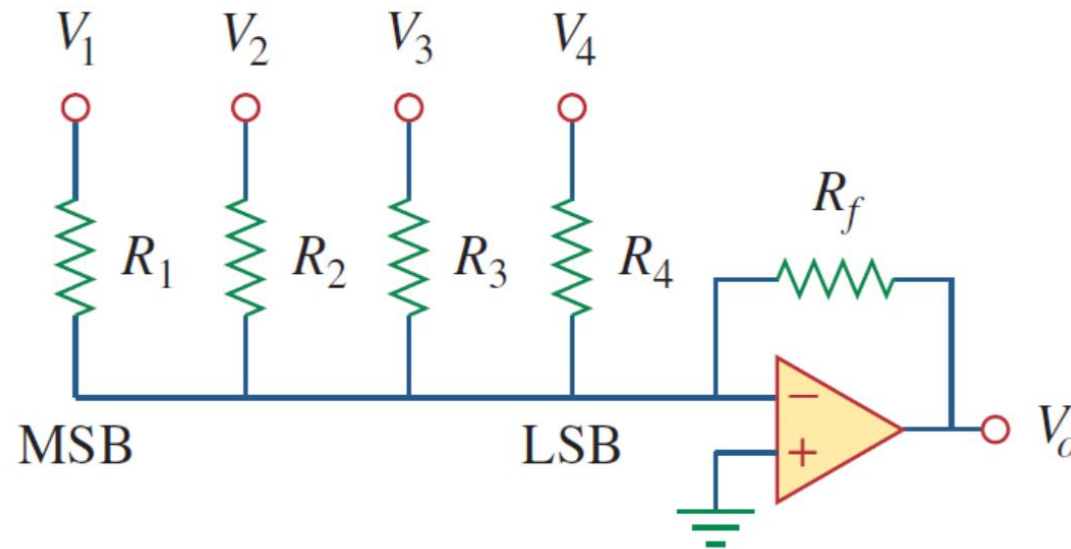

- Digital inputs:  $V_1 - V_4$  is 0 or 1V
- Input =  $[V_1 V_2 V_3 V_4]$
- $V_1$ : most significant bit (MSB)
- $V_4$ : least significant bit (LSB)

# DAC: binary weighted ladder

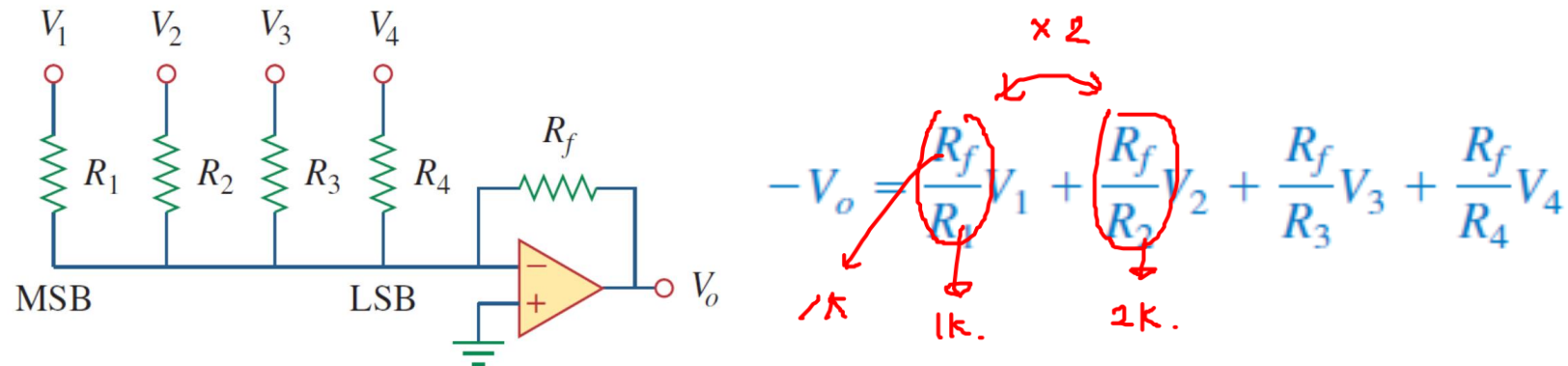


- **Bits are weighted** by descending value of  $R_f/R_n$  to produce 2 times difference for adjacent bits

➡ 
$$-V_o = k(2^3V_1 + 2^2V_2 + 2^1V_3 + 2^0V_4)$$

$kV_4$
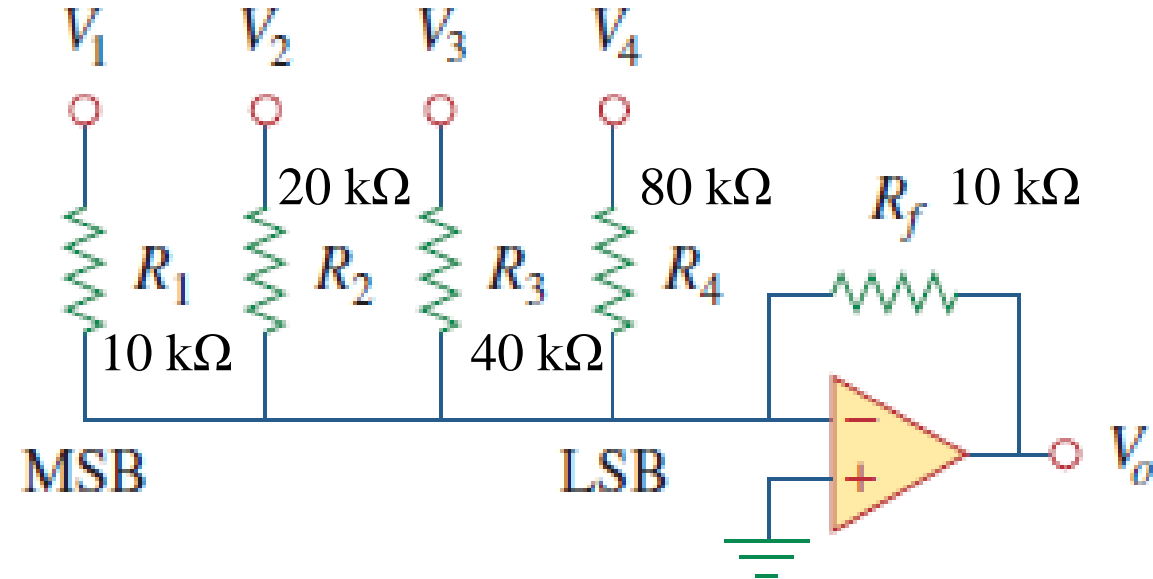
### Example 5.12


In the op amp circuit of Fig. 5.36(b), let  $R_f = 10\text{ k}\Omega$ ,  $R_1 = 10\text{ k}\Omega$ ,  $R_2 = 20\text{ k}\Omega$ ,  $R_3 = 40\text{ k}\Omega$ , and  $R_4 = 80\text{ k}\Omega$ . Obtain the analog output for binary inputs [0000], [0001], [0010], ..., [1111].



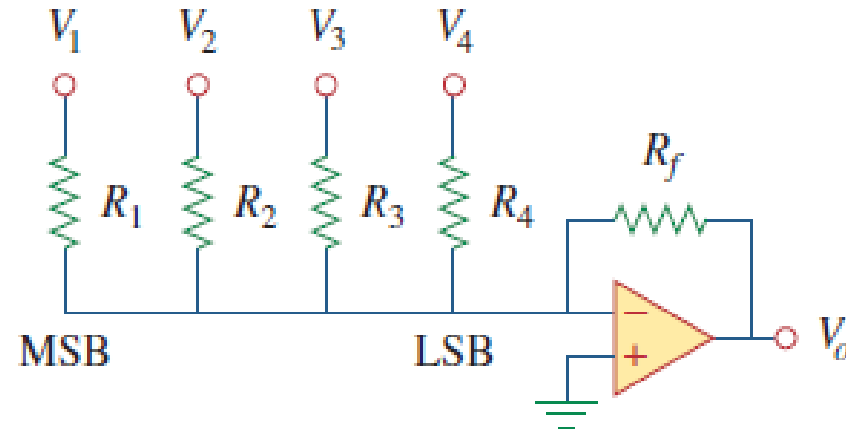1. Output voltage

$$\begin{aligned} -V_o &= \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 + \frac{R_f}{R_4} V_4 \\ &= V_1 + 0.5V_2 + 0.25V_3 + 0.125V_4 \end{aligned}$$





1. Output voltage

$$-V_o = \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 + \frac{R_f}{R_4} V_4$$

$$= V_1 + 0.5V_2 + 0.25V_3 + 0.125V_4$$

2. Digital input  $[V_1 V_2 V_3 V_4] = [0000]$  produces analog output  $-V_o = 0 \text{ V}$

$$[0001] \rightarrow -V_o = 0.125 \text{ V}$$

*increase 0.125 = LSB = resolution*

$$[0010] \rightarrow -V_o = 0.250 \text{ V}$$

$$[0011] \rightarrow -V_o = 0.375 \text{ V}$$

**TABLE 5.2**

Input and output values of the four-bit DAC.

Binary input [V <sub>1</sub> V <sub>2</sub> V <sub>3</sub> V <sub>4</sub> ]	Decimal value	Output -V <sub>o</sub>
0000	0	0
0001	1	0.125
0010	2	0.25
0011	3	0.375
0100	4	0.5
0101	5	0.625
0110	6	0.75
0111	7	0.875
1000	8	1.0
1001	9	1.125
1010	10	1.25
1011	11	1.375
1100	12	1.5
1101	13	1.625
1110	14	1.75
1111	15	1.875

Output 2V  
resolution 0.125 V × 16 = 2V

÷ 0.125



× 0.125

1.1V  
1.45V

≈ 2V

- Resolution (the smallest resolvable analog output) =  $0.125 \text{ V} = V_{\text{LSB}}$

**Question:** In practice, for 1 V range, if you want to produce a resolution of 1mV, roughly how many bits do you need?

~~forward~~

$$\begin{aligned} \text{output} &= 1000\text{mV} \\ \text{resolution} &= 1\text{mV} \end{aligned} \quad \uparrow \times 1000 = 2^{10}$$

**Question:** In practice, for 1 V range, if you want to produce a resolution of 1mV, roughly how many bits do you need?

For an n-bit DAC it can be given as

Resolution =  $\frac{V_{oFS}}{2^n - 1}$  where  $V_{oFS}$  = full scale output voltage.

$$0.001 = \frac{1}{2^n - 1}$$