


## 1 Superposition

## Steps


1. Only consider one **independent** source.
  - ▶ voltage source: short circuit
  - ▶ current source: open circuit
2. Use additivity.

↑  
More Exercises

## Example :

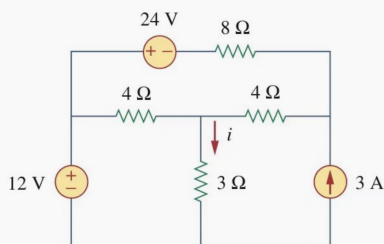Find  $i$  in the circuit.


Answer: 3A

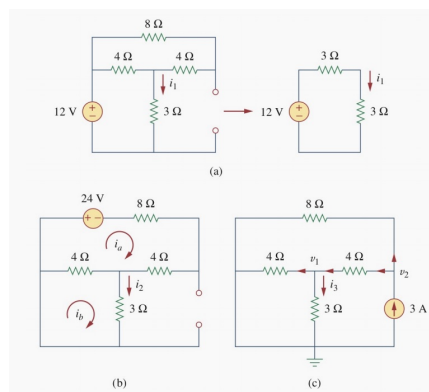
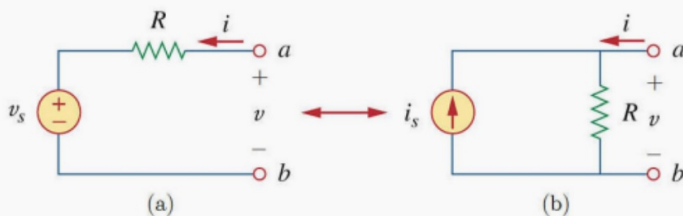
## 2 Source Transformations

We can replace a voltage source with a resistance with a corresponding current source with the same resistance to simplify the circuit.

In the case shown below,  $v_s = i_s \times R$




direction!

For dependent sources, the source transformation is also valid.

### 3 Thevenin's theorem

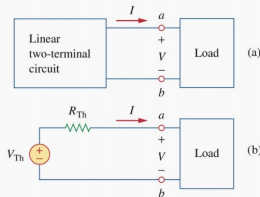
#### Thevenin's Theorem

A linear two-terminal circuit can be replaced by an equivalent circuit consisting of a voltage source  $V_{Th}$  in series with a resistor  $R_{Th}$ .



- $V_{Th}$ : the open-circuit voltage at the terminals.
- $R_{Th}$ : the equivalent resistance at the terminals when all the **independent sources** are turned off.

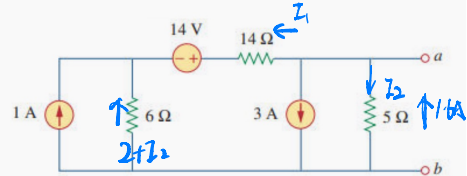Obtain the Thevenin equivalent circuit of this circuit with respect to terminal a and b.




Answer:  $V_{Th} = -8\text{ V}$   
 $R_{Th} = 4\Omega$

pay attention to the sign of the voltage !

$$\begin{aligned} I_1 + I_2 + 3 &= 0 \\ +14I_1 - 5I_2 - 6(2 + I_2) + 14 &= 0 \\ I_1 &= -1.4\text{ A} \quad I_2 = -1.6\text{ A} \end{aligned}$$
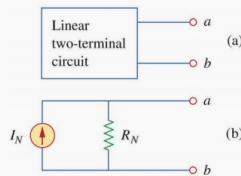
### 4 Norton's theorem

A linear two-terminal circuit can be replaced by an equivalent circuit consisting of a current source  $I_{Th}$  in parallel with a resistor  $R_{Th}$ .




- $I_{Th}$ : the short-circuit current at the terminals.
- $R_{Th}$ : the equivalent resistance at the terminals when all the **independent sources** are turned off.

### 5 Maximum power transfer

A circuit is usually designed to provide power to a load. For different kinds of circuits, we have different concerns

- **Maximum Power Efficiency:** In power utility systems, the amount of electricity is very large. Therefore, how to **increase the efficiency of power transfer** becomes an important problem.
- **Maximum Power Transfer:** In communication and instrumental systems, the amount of electricity is small so the problem of efficiency is not so important. Instead, we want to **transfer as much of power as possible to the load.**

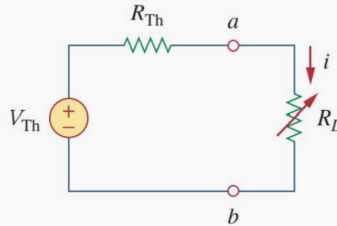The Thevenin's equivalent circuit is useful in finding the maximum power delivered to a load. In the circuit below,  $R_L$  represents the load.



Since

$$p = i^2 R_L = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

Let  $\frac{dP}{dR_L} = V_{Th}^2 \frac{R_{Th} - R_L}{(R_{Th} + R_L)^3} = 0$ , we have  $R_L = R_{Th}$ .

And when  $R_L = R_{Th}$ ,  $\frac{d^2 P}{dR_L^2} = V_{Th}^2 \frac{2R_L - 4R_{Th}}{(R_{Th} + R_L)^4} = -\frac{V_{Th}^2}{8R_{Th}^2} < 0$ .

Thus  $p$  reaches maximum at  $R_L = R_{Th}$ .  $p_{max} = \frac{V_{Th}^2}{4R_{Th}}$

## 6 Ideal Op-amp

Characteristics of ideal op-amp:

- ▶ Open circuit at two input terminals ( $i_1 = i_2 = 0$ )
- ▶ Same voltage at two input terminals ( $v_1 = v_2$ )
- ▶ Do not apply KCL to the output terminals!

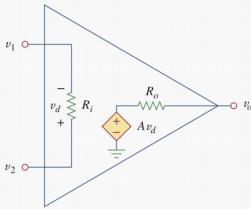


Figure: Op-amp's equivalent circuit



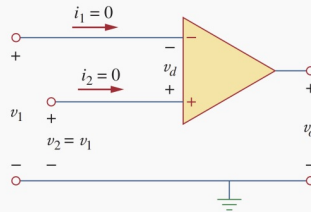


Figure: Symbol of ideal op-amp


### Inverting Amplifier

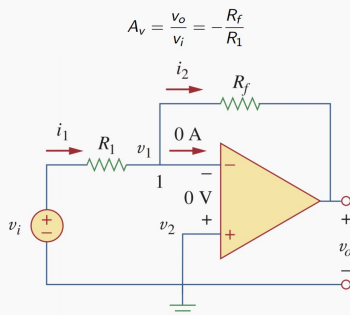

### Non-inverting Amplifier

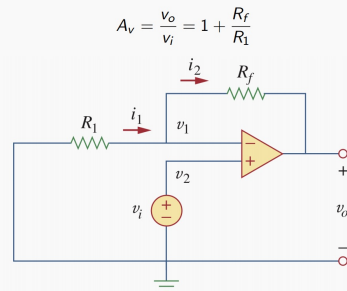


## Summing Amplifier

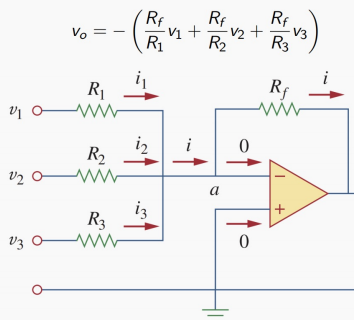
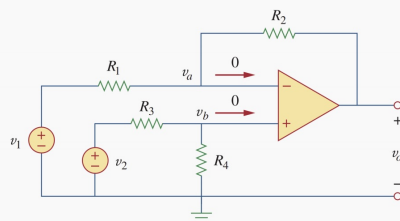
## Difference Amplifier


Check if  $R_1 = R_2$ ,  $R_3 = R_4$

$$v_o = \left( \frac{R_2}{R_1} + 1 \right) \frac{R_4}{R_3 + R_4} v_2 - \frac{R_2}{R_1} v_1$$



## Cascaded Op Amps

### Gain of Cascaded Op Amp

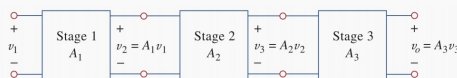

Original input signal is increased by the gain of the individual stage, and the final gain is the **product of all gains at each stage**.


$$A = \frac{v_o}{v_1} = \frac{v_2}{v_1} \cdot \frac{v_3}{v_2} \cdot \frac{v_o}{v_3} = A_1 A_2 A_3$$

For basic op-amp circuits:

| Op-amp circuits         | Input-output relationship                                                                                                                     |
|-------------------------|-----------------------------------------------------------------------------------------------------------------------------------------------|
| Inverting amplifier     | $A = \frac{v_o}{v_i} = -\frac{R_f}{R_1}$                                                                                                      |
| Non-inverting amplifier | $A = \frac{v_o}{v_i} = 1 + \frac{R_f}{R_1}$                                                                                                   |
| Summing amplifier       | $v_o = - \left( \frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3 \right)$                                                      |
| Difference amplifier    | $v_o = \left[ \left( \frac{R_2}{R_1} + 1 \right) \left( \frac{R_4/R_3}{1 + R_4/R_3} \right) \right] v_2 - \left[ \frac{R_2}{R_1} \right] v_1$ |

## 7 Exercises

0 Show that:

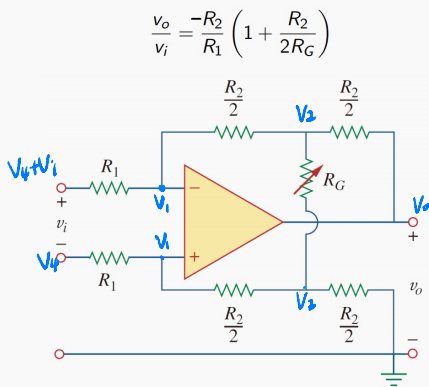

$$\left\{ \begin{aligned} \frac{V_1 - (V_4 + V_i)}{R_1} + \frac{V_1 - V_2}{\frac{R_1}{2}} &= 0 \quad (i_1=0) \end{aligned} \right. \quad (1)$$

$$\left\{ \begin{aligned} \frac{V_1 - V_4}{R_1} + \frac{V_1 - V_2}{\frac{R_1}{2}} &= 0 \quad (i_2=0) \end{aligned} \right. \quad (2)$$

$$(1) - (2): -\frac{V_i}{R_1} - \frac{2(V_2 - V_3)}{R_2} = 0$$

$$\Rightarrow V_i = -\frac{2R_1}{R_2} (V_2 - V_3)$$

$$\left\{ \begin{aligned} \frac{V_2 - V_1}{\frac{R_2}{2}} + \frac{V_2 - V_3}{R_4} + \frac{V_2 - V_0}{\frac{R_2}{2}} &= 0 \end{aligned} \right.$$

$$\frac{V_2 - V_1}{\frac{R_2}{2}} + \frac{V_2 - V_3}{R_4} + \frac{V_2}{\frac{R_2}{2}} = 0$$

$$\frac{2V_2}{R_2} + \frac{V_2 - V_3}{R_4} + \frac{2(V_2 - V_0)}{R_2} = \frac{2V_2}{R_2} + \frac{V_2 - V_0}{R_4} + \frac{2V_2}{R_2}$$

$$\Rightarrow V_0 = \left(2 + \frac{R_2}{R_4}\right) (V_2 - V_3)$$

$$\frac{V_0}{V_i} = -\frac{R_2}{R_1} \left(1 + \frac{R_2}{2R_4}\right)$$

②


4. Suppose all resistors without labels have resistance of  $R$ . Please answer the following questions.

[16 points]

(1)  $V_1$  in terms of  $V_s$  and  $R$ .

(2) The equivalent resistance  $R_{ab}$  between terminals  $a$  and  $b$ .

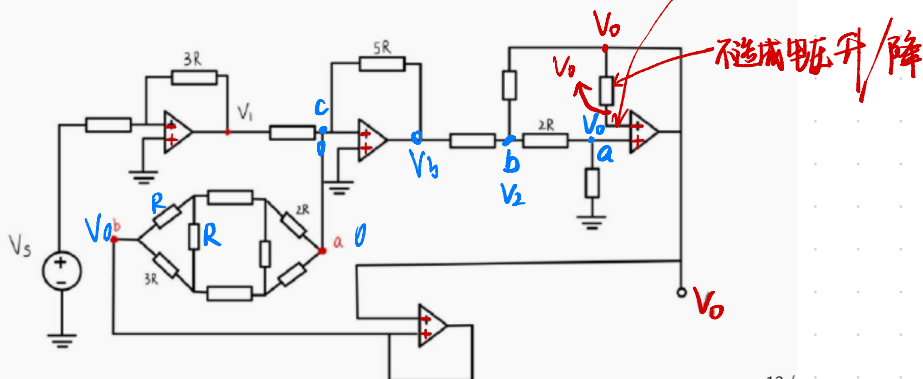(3) The overall gain  $G = \frac{V_0}{V_s}$ .



13 /

(1) voltage Amp

$$V_1 = -\frac{3R}{R} V_s = -3V_s$$



$$R_{ab} = \frac{3}{5}R + (\frac{1}{5}R + R + 3R) \parallel (\frac{3}{5}R + R + \frac{1}{5}R) + \frac{1}{5}R$$

$$= \frac{141}{71}R = 1.986R$$

(3)

$$\begin{array}{l} \text{node a} \\ \text{node b} \\ \text{node c} \end{array} \left\{ \begin{array}{l} \frac{V_0 - V_3}{2R} + \frac{V_0}{R} = 0 \\ \frac{V_3 - V_0}{R} + \frac{V_0 - V_0}{R} + \frac{V_0}{2R + R} = 0 \\ \frac{2V_s}{R} - \frac{V_3}{5R} - \frac{V_0}{\frac{141}{71}R} = 0 \end{array} \right.$$

$$\Rightarrow V_3 = 6V_0$$

$$2V_s - \frac{6}{5}V_0 - \frac{71}{141}V_0 = 0$$

$$\frac{V_0}{V_s} = \frac{2115}{1201} = 1.76$$